

# Hardware Synthesis from Bluespec

*Silvina Hanono Wachman*

Computer Science & Artificial Intelligence Lab.  
Massachusetts Institute of Technology


Happy 🥧 Day!

# Guarded interfaces

- Modules with guarded interfaces are a new way of expressing sequential circuits
- Every method has a *guard* (*rdy wire*)
  - For some methods guard is always true
- The value returned by a method is meaningful only if its guard is true
- Every action method has an *enable signal* (*en wire*) and it can be invoked (en can be set to true) only if its guard is true
- Every method can have input data
- Value and ActionValue methods have output data


```
interface Fifo#(numeric type size, type t);  
  method Action enq(t x);  
  method Action deq;  
  method t first;  
endinterface
```

 notice, *en* and *rdy* wires are implicit


 
# GCD Interface

```
interface GCD;  
  method Action start (Bit#(32) a, Bit#(32) b);  
  method ActionValue#(Bit#(32)) getResult;  
endinterface
```



```
module mkGCD (GCD);
```

```
  Reg#(Bit#(32)) x <- mkReg(0); Reg#(Bit#(32)) y <- mkReg(0);  
  Reg#(Bool) busy_flag <- mkReg(False);
```

```
  rule gcd;
```

```
    if (x >= y) begin x <= x - y; end //subtract
```

```
    else if (x != 0) begin x <= y; y <= x; end //swap
```

```
  endrule
```

```
  method Action start(Bit#(32) a, Bit#(32) b) if(!busy_flag);
```

```
    x <= a; y <= b; busy_flag <= True;
```

```
  endmethod
```

```
  method ActionValue#(Bit#(32)) getResult if(busy_flag&&(x==0));
```

```
    busy_flag <= False; return y;
```


```
  endmethod
```

```
endmodule
```

# Power of Abstraction:

## Another GCD implementation

---

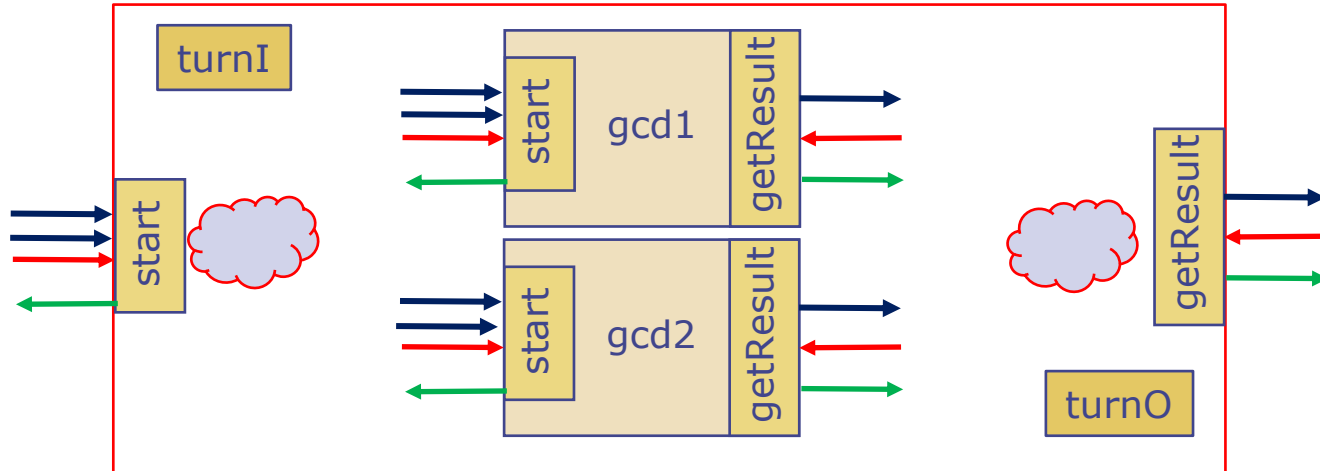

- A GCD module with the same interface but with twice the throughput; uses two gcd modules in parallel
- turnI is used by the start method to direct the input to the gcd whose turn it is and then turnI is flipped
- Similarly, turnO is used by getResult to get the output from the appropriate gcd, and then turnO is flipped

```
interface GCD;  
    method Action start (Bit#(32) a, Bit#(32) b);  
    method ActionValue#(Bit#(32)) getResult;  
endinterface
```

# High-throughput GCD code

```
module mkMultiGCD (GCD);
```

```
  GCD gcd1 <- mkGCD();
```

```
  GCD gcd2 <- mkGCD();
```

```
  Reg#(Bool) turnI <- mkReg(False);
```

```
  Reg#(Bool) turnO <- mkReg(False);
```

```
  method Action start(Bit#(32) a, Bit#(32) b);
```

```
    if (turnI) gcd1.start(a,b); else gcd2.start(a,b);
```

```
    turnI <= !turnI;
```

```
  endmethod
```

```
  method ActionValue (Bit#(32)) getResult;
```

```
    Bit#(32) y;
```

```
    if (turnO) y <- gcd1.getResult
```


```
    else y <- gcd2.getResult;
```

```
    turnO <= !turnO
```

```
    return y;
```

```
  endmethod
```

```
endmodule
```

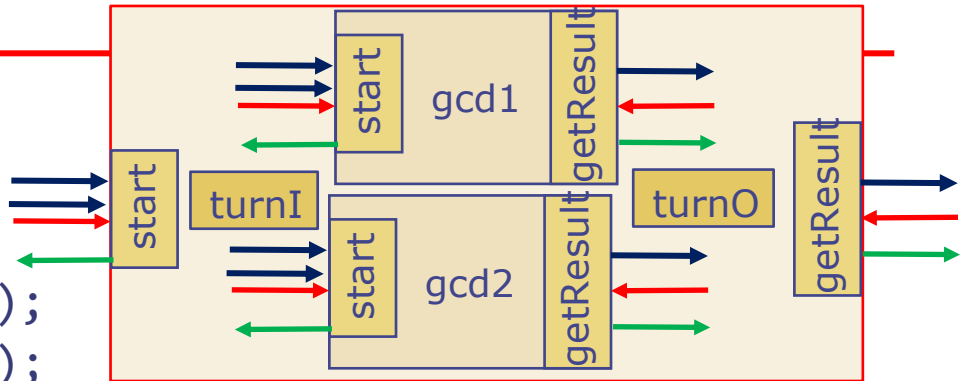

```
interface GCD;
```

```
  method Action start (Bit#(32) a, Bit#(32) b);
```


```
  method ActionValue#(Bit#(32)) getResult;
```

```
endinterface
```


# Hardware Synthesis

How is Bluespec code synthesized into hardware?
 
# A new mux-like structure to deal with multiple sources


 
$$x = (v_1 \ \& \ x_1) \mid (v_2 \ \& \ x_2)$$
$$v = v_1 \mid v_2$$



- $x_i$  has a meaningful value only if its corresponding  $v_i$  is true
- Compiler has to ensure that at most one  $v_i$  input to the mux is true at any given time; the circuit will behave unpredictably if multiple input signals are valid


# FIFO Circuit

```

module mkFifo (Fifo#(1, t));
  Reg#(t)    d  <- mkRegU;
  Reg#(Bool) v  <- mkReg(False);
  method Action enq(t x) if (!v);
    v <= True; d <= x;
  endmethod
  method Action deq if (v);
    v <= False;
  endmethod
  method t first if (v);
    return d;
  endmethod
endmodule

```

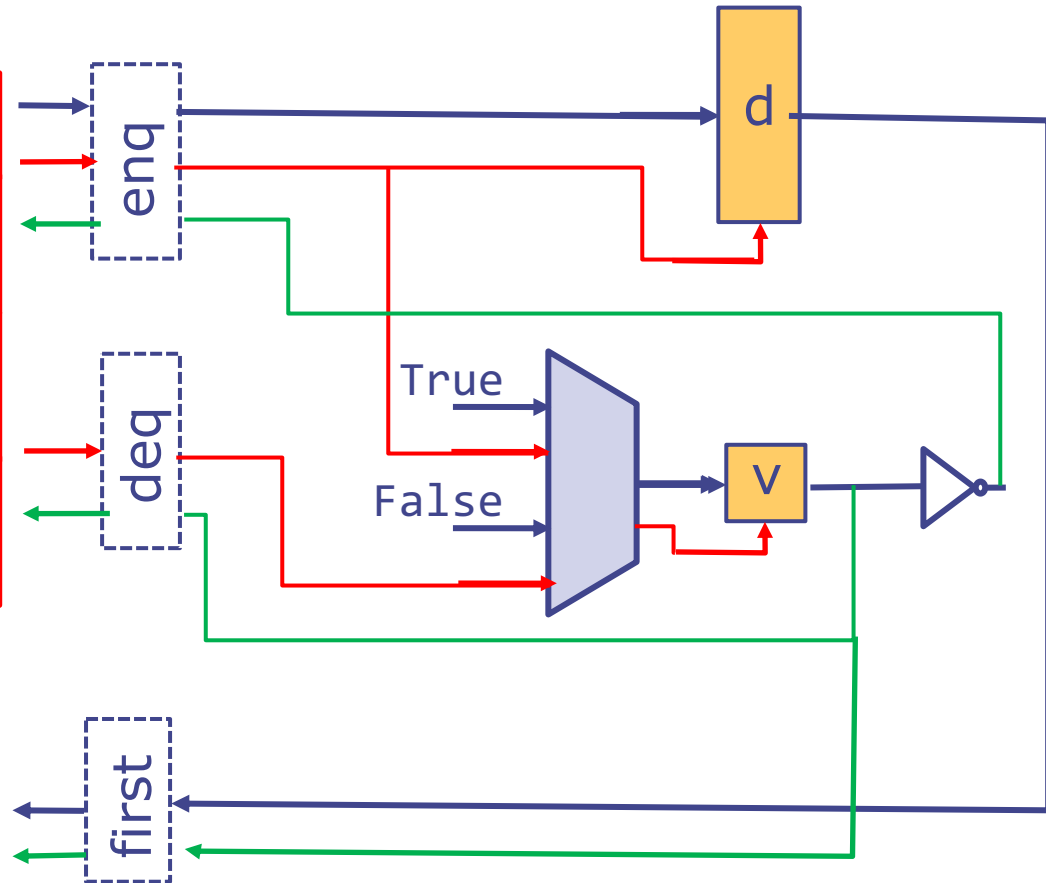- I/O: Interface
- Instantiate state
- For every register with multiple assignments, insert a mux
- Compile enq
- Compile deq
- Compile first




```

interface Fifo#(numeric type size, type t);
  method Action enq(t x);
  method Action deq;
  method t first;
endinterface

```



# Redrawing the FIFO Circuit

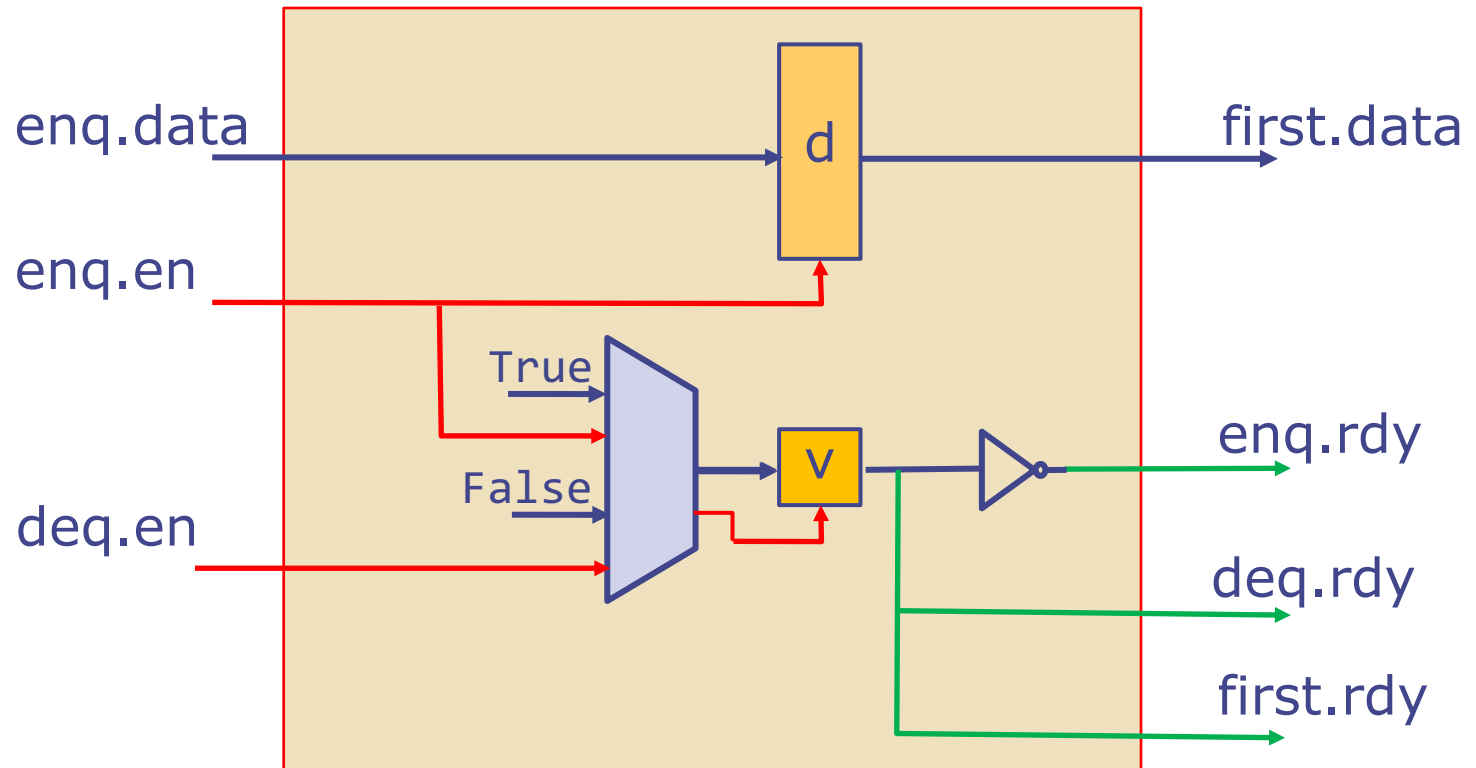

A module is a sequential circuit with input and output wires corresponding to its interface methods

This is a sequential circuit because it has state elements; however, it has no cycles

# Next state transition

## Partial Truth Table


An aside

inputs			state		next state		outputs			
enq. en	enq. data	deq. en	$d^t$	$v^t$	$d^{t+1}$	$v^{t+1}$	enq. rdy	deq. rdy	first. rdy	first. data
0	x	0	x	0	x	0	1	0	0	-
1	d	0	x	0	d	1	0	1	1	-
0	x	0	d	1	d	1	0	1	1	d
0	x	1	d	1	-	0	1	0	0	d
1				1			0			
		1		0				0		
1		1		0			1			
1		1		1				1		


Illegal inputs

Tedious!

# Streaming a function: Circuit

 

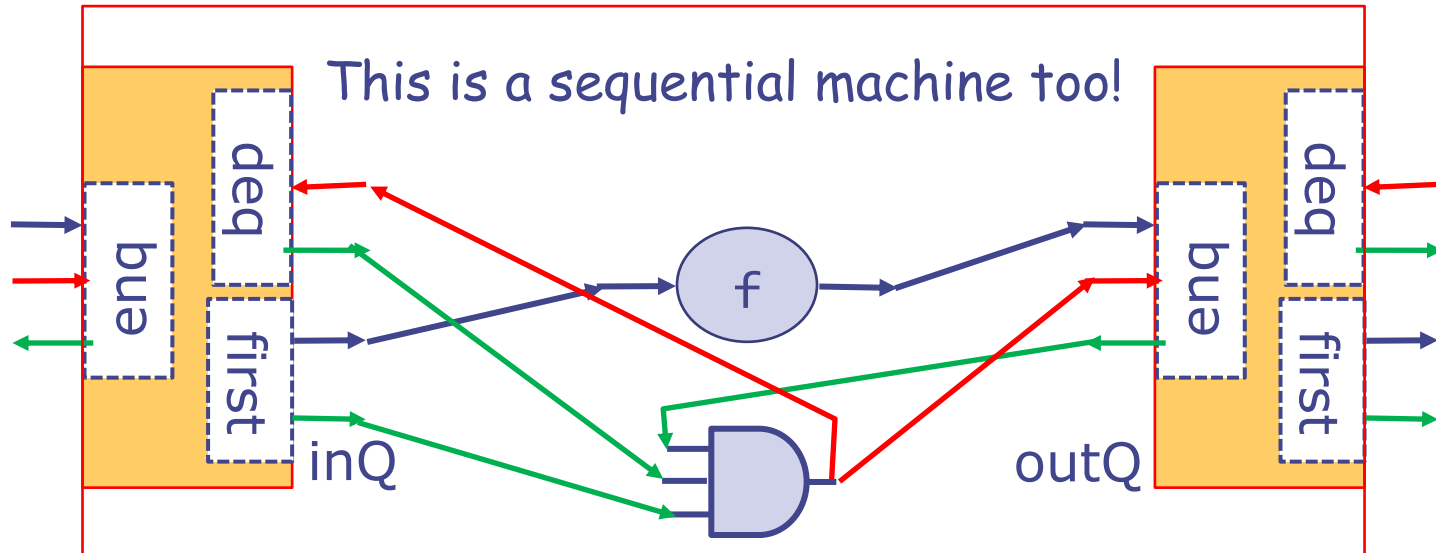
```
rule stream;
    outQ.enq(f(inQ.first));
    inQ.deq;
endrule
```



- Connect the datapath
- Collect the ready signals
- Enable the called methods

Notice that `enq.en` cannot be `True` unless `enq.rdy` is `true`; `deq.en` cannot be `True` unless `deq.rdy` is `true`

# Redrawing the sequential circuit

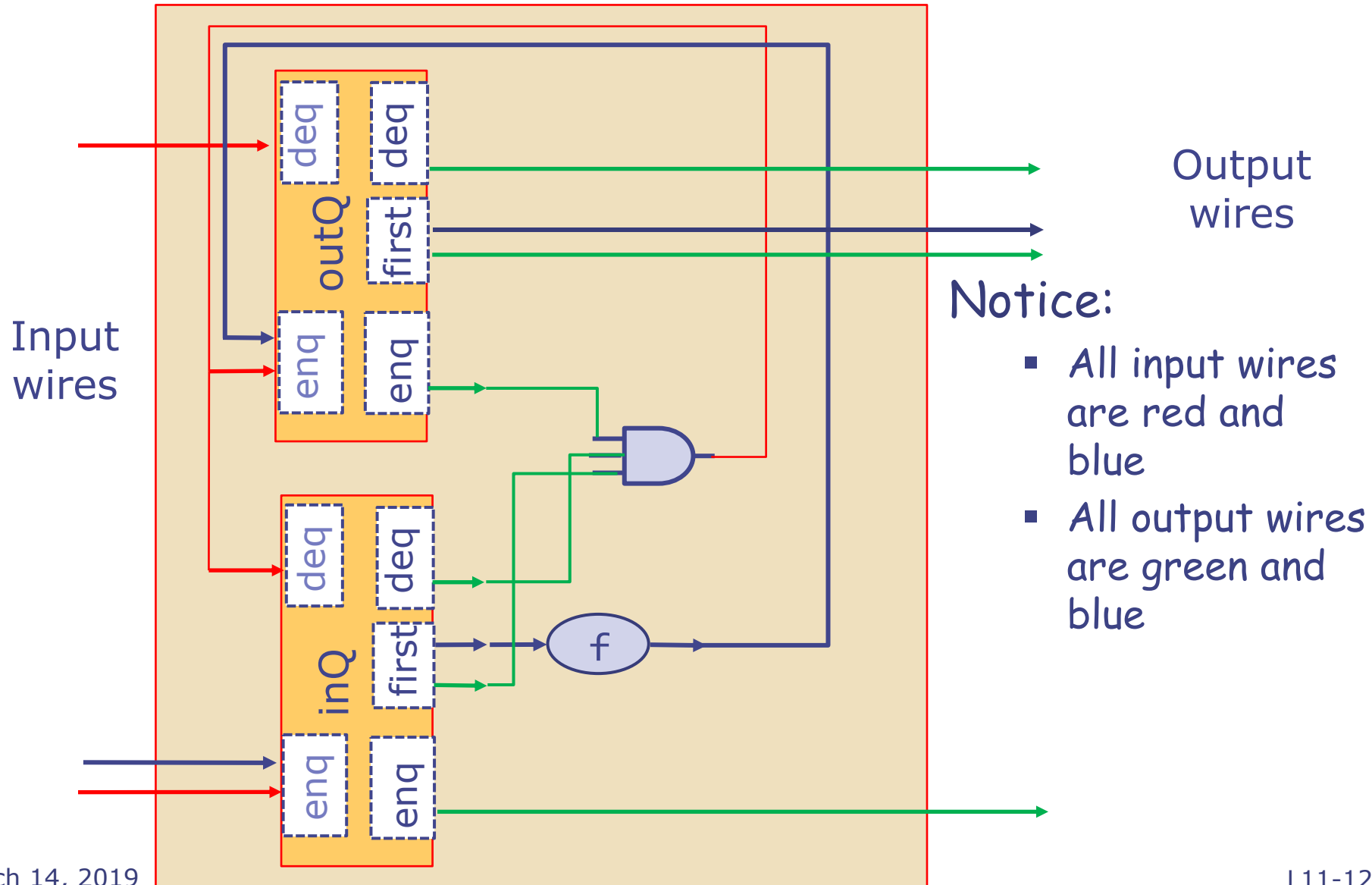


# Hierarchical sequential circuits
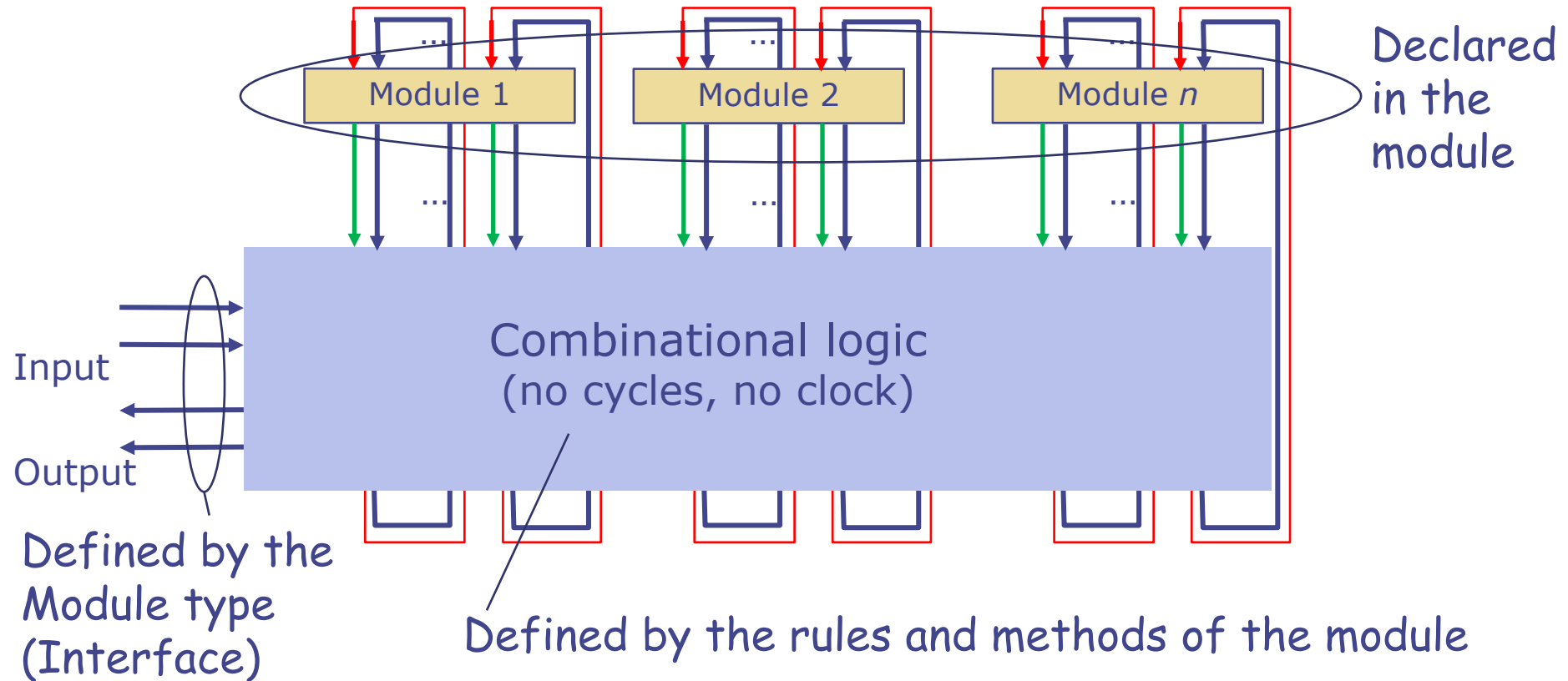
## sequential circuits containing modules

---

Each module represents a sequential machine



# Hardware Synthesis

## High-level idea


---

- Every module represents a sequential machine
- Register is a primitive module – its implementation is outside the language
  - Register bit width is derived from its type
- Each Register and module is instantiated explicitly
- Input/Output wires of a module are derived from its interface, i.e., type
- Rules and methods define the combinational logic to connect registers and modules

The resulting hardware is a collection of sequential machines, which itself behaves like a sequential machine
 
# Register: The Primitive module

```
interface Reg#(type t);  
  method Action _write(t x);  
  method t _read;  
endinterface
```




- Implementation is defined outside the language
- A register is created using `mkReg` or `mkRegU`
- The guards of `_write` and `_read` are always true and not generated
- Special syntax
  - `x <= e` instead of `x._write(e)`
  - `x` instead of `x._read` in expressions

# Interface defines input/output wires

---

- Inputs and outputs are defined by the *type* of the module, i.e., its interface definition
  - Each *method* has a output **ready** wire
  - Each *method* may have 0 or more input data wires
  - Each *Action method* and *ActionValue method* has an input **enable** wire
  - Each *value method* and *ActionValue method* has an output data wire
  - An *Action method* has no output data wire
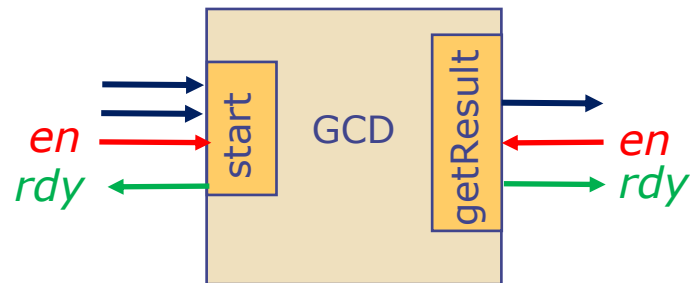
```
interface GCD;  
  method Action start  
    (Bit#(32) a, Bit#(32) b);  
  method ActionValue(Bit#(32))  
    getResult;  
endinterface
```






# Compiling Guards

---


- Bluespec design specifies the guard for each method and rule
  - The guard may be stated explicitly; If there is no guard then it is assumed to be true
  - But the guard also implicitly inherits the guards of the called methods
  - The compiler generates the ready signal from these explicit and implicit guards
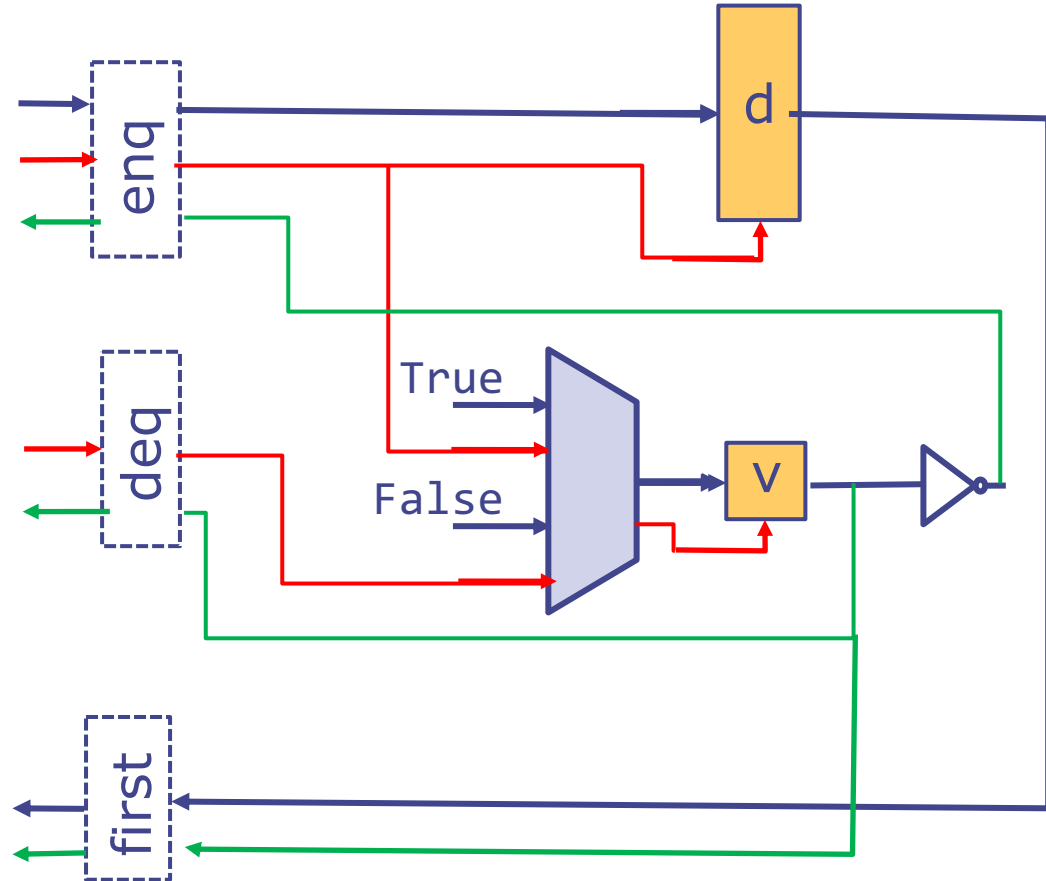
# Guards define the ready signals


```
module mkFifo (Fifo#(1, t));  
  Reg#(t)    d  <- mkRegU;  
  Reg#(Bool) v  <- mkReg(False);  
  method Action enq(t x) if (!v);  
    v <= True; d <= x;  
  endmethod  
  method Action deq if (v);  
    v <= False;  
  endmethod  
  method t first if (v);  
    return d;  
  endmethod  
endmodule
```



# Combined Guards

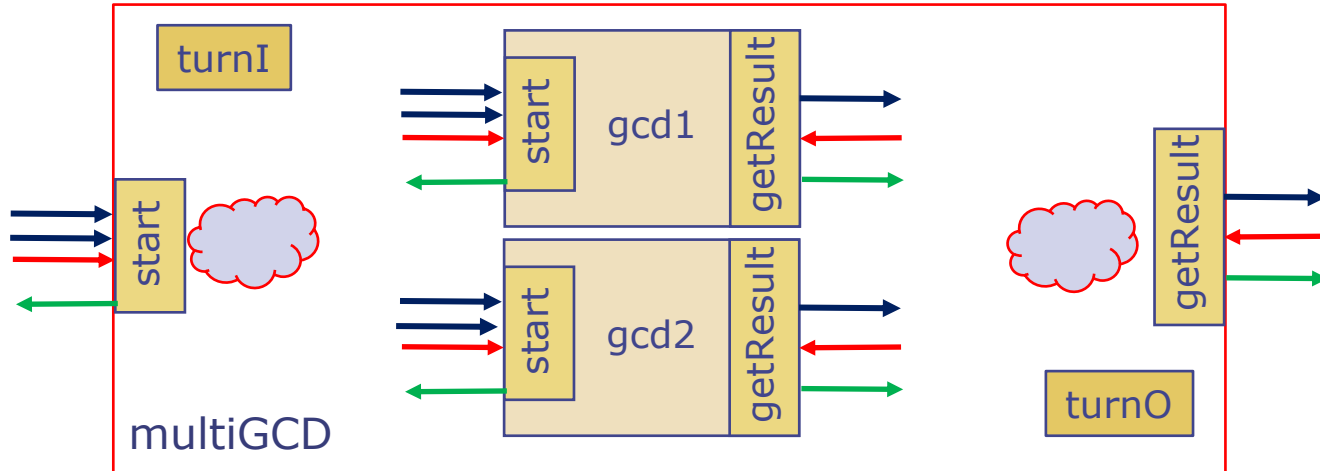

 
```
method Action start(Bit#(32) a, Bit#(32) b);  
  if (turnI) gcd1.start(a,b);  
  else gcd2.start(a,b);  
  turnI <= !turnI;  
endmethod
```


 
# Generating enable signals and associated data

---

- Bluespec design *implicitly* specifies the enable signal for each of the called Action and ActionValue method
- It does so by propagating the incoming enable signals of the calling method or rule






# Rules and methods define the combinational logic and enables

```
module mkEx1 (...);  
  Reg#(t) x <- mkRegU;  
  method Action f(t a);  
    x <= e;  
  endmethod endmodule
```

```
module mkEx2 (...);  
  Reg#(t) x <- mkRegU;  
  method Action f(t a);  
    if (b) x <= e;  
  endmethod endmodule
```


```
module mkEx3 (...);  
  Reg#(t) x <- mkRegU;  
  method Action f(t a);  
    if (b) x <= e1;  
    else x <= e2;  
  endmethod  
endmodule
```

Not shown:  
**f.rdy = True**

   
 
# Synthesis of multiple sources for register assignments

```
module mkEx4 (...);  
  Reg#(t) x <- mkRegU;  
  method Action f(t a);  
    x <= e1;  
  endmethod  
  method Action g(t a);  
    x <= e2;  
  endmethod  
endmodule
```



- Compiler has to ensure that both *f* and *g* can't be enabled together
- This information is provided by the compiler in the form of a *conflict matrix* (CM) for each module

# Conflict Matrix for an Interface

---

- Conflict Matrix (CM) defines which methods of a module can be called concurrently
- CM for a register:

	reg.r	reg.w
reg.r	CF	<
reg.w	>	C

  - Two reads can be performed concurrently (CF – Conflict Free)
  - Two concurrent writes conflict (C) and are not permitted
  - A read and a write can be performed concurrently and it behaves as if the read happened before the write ( $r < w$ )
- CM of a register is used systematically to derive the CM for the interface of a module

*CM can also be defined for any set of rules*


# One-Element FIFO

```

module mkFifo (Fifo#(1, t));
  Reg#(t)      d  <- mkRegU;
  Reg#(Bool)   v  <- mkReg(False);
  method Action enq(t x) if (!v);
    v <= True; d <= x;
  endmethod
  method Action deq if (v);
    v <= False;
  endmethod
  method t first if (v);
    return d;
  endmethod
endmodule

```

 We don't care about conflicts between mutually exclusive rules or methods because they can never be ready at the same time



	enq	deq	first
enq	C	ME	ME
deq	ME	C	>
first	ME	<	CF

ME = mutually exclusive  
 $a < b$  = a precedes b



# Take-home problem: Draw the circuit for this GCD

```
module mkGCD (GCD);  
  Reg#(Bit#(32)) x <- mkReg(0);  
  Reg#(Bit#(32)) y <- mkReg(0);  
  Reg#(Bool) busy <- mkReg(False);  
  rule gcd;  
    if (x >= y) begin x <= x - y; end //subtract  
    else if (x != 0) begin x <= y; y <= x; end //swap  
  endrule  
  method Action start(Bit#(32) a, Bit#(32) b) if (!busy);  
    x <= a; y <= b; busy <= True;  
  endmethod  
  method ActionValue (Bit#(32)) getResult if (busy && (x==0));  
    busy <= False; return y;  
  endmethod  
endmodule
```

```
interface GCD;  
  method Action start  
    (Bit#(32) a, Bit#(32) b);  
  method ActionValue(Bit#(32))  
    getResult;  
endinterface
```

Assume b != 0

