

Sequential Circuits: Modules with Guarded Interfaces

Arvind

Computer Science & Artificial Intelligence Lab
M.I.T.

Types of Methods


- *Value method*: don't update the state of the module, only observe the internal state
 - example: `mod4counter.read`, `gcd.busy`, `gcd.ready`
- *Action method*: Only updates the state of the module, doesn't return any value
 - example: `mod4counter.inc`, `gcd.start`
 - The circuit for an Action method contains an *enable* wire, which must be true for the call to take effect
- *ActionValue#(t)*: Updates the state of the module *and* returns a value of type *t*.
 - example: `gcd.getResult`
 - The circuit for an ActionValue method contains an *enable* wire, which must be true for the call to take effect

All methods can have input arguments e.g. `gcd.start(x,y)`

Method calls

- Value method
 - `let counterValue = mod4counter.read;`
 - `Bool isGcdBusy = gcd.busy;`
- Action method
 - `mod4counter.inc;`
 - `gcd.start(13,27);`
- `ActionValue#(t)`
 - `let resultGcd <- gcd.getResult;`
 - Notice the use of `<-` instead of `=`
 - Suppose we wrote
 - `let badResultGCD = gcd.getResult;`
 - then the type of `badResultGCD` would be `ActionValue#(t)` instead of `t`.
 - `=` just names the value on the right hand side while `<-` indicates a side effect in addition to a return value

GCD implementation

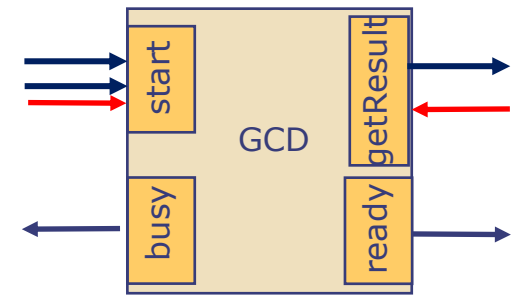

Instantiate state

```
module mkGCD (GCD); Type
```

```
  Reg#(Bit#(32)) x <- mkReg(0); Reg#(Bit#(32)) y <- mkReg(0);
  Reg#(Bool) busy_flag <- mkReg(False);
```

```
  rule gcd; Rule gcd executes repeatedly until x becomes 0
```

```
    if (x >= y) begin x <= x - y; end //subtract
```

```
    else if (x != 0) begin x <= y; y <= x; end //swap
```

```
  endrule
```

```
  method Action start(Bit#(32) a, Bit#(32) b) ;
```

```
    x <= a; y <= b; busy_flag <= True;
```

```
  endmethod
```

```
  method ActionValue#(Bit#(32)) getResult ;
```

```
    busy_flag <= False; return y;
```

```
  endmethod
```

```
  method Bool busy
```

```
    = busy_flag;
```

```
  method Bool ready
```

```
    = (x==0);
```

```
endmodule
```

Assume b != 0

start should be called only if the busy is false;
getResult should be called only when ready is true.

```
interface GCD;
```

```
  method Action start(Bit#(32) a, Bit#(32) b);
```

```
  method ActionValue#(Bit#(32)) getResult;
```

```
  method Bool busy;
```

```
  method Bool ready;
```

```
endinterface
```

Rule

A module may contain rules

```
rule gcd;  
  if (x >= y) begin x <= x - y; end //subtract  
  else if (x != 0) begin  $x^{t+1} \leq y^t$ ;  $y^{t+1} \leq x^t$ ; end //swap  
endrule
```

What is meaning of this?

Swap!

- A rule has a name (e.g., gcd)
- A rule is a collection of actions, which invoke methods
- All actions in a rule execute in parallel
- A rule can execute any time and when it executes all of its actions must execute

atomicity

Parallel Composition of Actions & Double-Writes

rule one;

y <= 3; x <= 5; x <= 7; endrule

Double write

rule two;

y <= 3; if (b) x <= 7; else x <= 5; endrule

No double write

rule three;


y <= 3; x <= 5; if (b) x <= 7; endrule

Possibility of a double write

- Parallel composition, and consequently a rule containing it, is illegal if a double-write possibility exists
- The Bluespec compiler **rejects** a program if there is any possibility of a double write in a rule or method

First-In-First-Out queue (FIFO)

- A fifo is an important data structure which is used extensively both in hardware and software to connect *things* together
- A producer enqueues values into the fifo
- A consumer dequeues values from the fifo
- Dequeued values come out in the same order in which they were enqueued (i.e. First In, First Out)
- In hardware, fifo have fixed size which is often as small as 1, and therefore the producer blocks when enqueueing into a full fifo and the consumer blocks when dequeueing from an empty fifo

 


FIFO in hardware

First-In-First-Out queue

```
interface Fifo#(numeric type size, type t);  
  method Bool notFull;  
  method Bool notEmpty;  
  method Action enq(t x);  
  method Action deq;  
  method t first;  
endinterface
```



Type of the data
stored in the FIFO

 - enq should be called only if notFull returns True;
- deq and first should be called only if notEmpty returns True



Interface of a module defines its type


An Implementation: One-Element FIFO

```
module mkFifo (Fifo#(1, t)) provisos (Bits#(t, tSz));  
  Reg#(t)      d  <- mkRegU;  Instantiate a data register  
  Reg#(Bool) v   <- mkReg(False);  Instantiate a valid bit  
  method Bool notFull;  
    return !v;  
  endmethod  
  method Bool notEmpty;  
    return v;  
  endmethod  
  method Action enq(t x);  
    v <= True; d <= x;  
  endmethod  
  method Action deq;  
    v <= False;  
  endmethod  
  method t first;  
    return d;  
  endmethod  
endmodule
```

Fifo can hold any type of data but
the type must be "bitifiable"

```
interface Fifo#(numeric type size, type t);  
  method Bool notFull;  
  method Bool notEmpty;  
  method Action enq(t x);  
  method Action deq;  
  method t first;  
endinterface
```

Streaming a function

 


```
rule stream;  
  if(inQ.notEmpty && outQ.notFull)  
    begin outQ.enq(f(inQ.first)); inQ.deq; end  
endrule
```

Boolean "AND" operation

Guarded interfaces

- Make the life of the programmers easier: Include some checks (readiness, fullness, ...) in the method definition itself, so that the user does not have to test the applicability of the method explicitly from outside
- Guarded Interface:
 - Every method has a *guard* (*rdy* wire)
 - The value returned by a method is meaningful only if its guard is true
 - Every action method has an *enable signal* (*en* wire) and it can be invoked (en can be set to true) only if its guard is true

 


```
interface Fifo#(numeric type size, type t);  
  method Action enq(t x);  
  method Action deq;  
  method t first;  
endinterface
```

notice, **en** and
rdy wires are
implicit


One-Element FIFO Implementation with guards
 
```
module mkFifo (Fifo#(1, t));  
  Reg#(t)      d  <- mkRegU;  
  Reg#(Bool) v  <- mkReg(False);  
  method Action enq(t x) if (!v);  
    v <= True; d <= x;  
  endmethod  
  method Action deq if (v);  
    v <= False;  
  endmethod  
  method t first if (v);  
    return d;  
  endmethod  
endmodule
```




Syntax: lack of semicolon turns the if into a guard

 Guard expression is what is connected to the rdy wire of a method



 
Streaming a function using a FIFO with guarded interfaces




```
rule stream;  
if(inQ.notEmpty && outQ.notFull)  
  begin outQ.enq(f(inQ.first)); inQ.deq; end  
endrule
```

The implicit guards of the method calls are sufficient because a rule can execute only if the guards of all of its method calls are true

GCD with and without guards

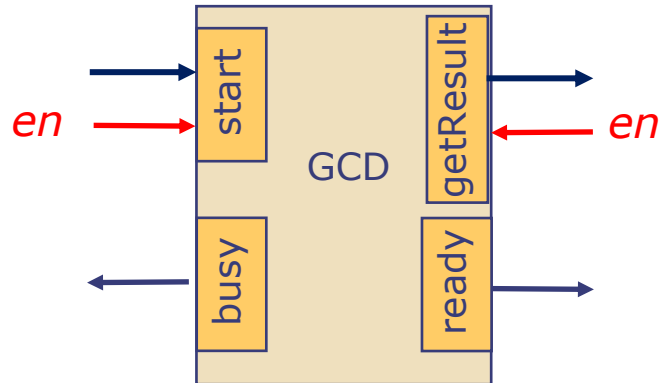

Interface without guards

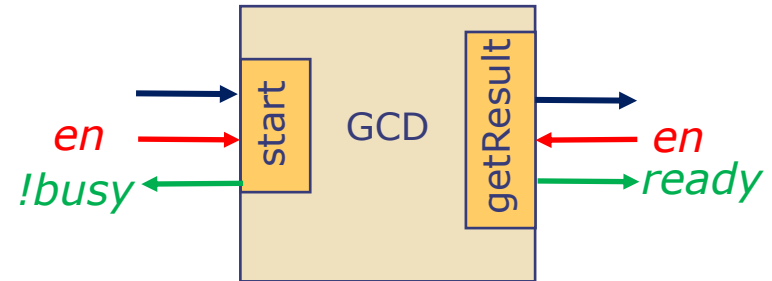

Interface with guards

```
interface GCD;  
  method Action start (Bit#(32) a, Bit#(32) b);  
  method ActionValue#(Bit#(32)) getResult;  
  method Bool busy;  
  method Bool ready;  
endinterface
```

- start should be called only if the module is not busy;
- getResult should be called only when ready is true

GCD with Guards

```
module mkGCD (GCD);
  Reg#(Bit#(32)) x <- mkReg(0); Reg#(Bit#(32)) y <- mkReg(0);
  Reg#(Bool) busy_flag <- mkReg(False);

  rule gcd;
    if (x >= y) begin x <= x - y; end //subtract
    else if (x != 0) begin x <= y; y <= x; end //swap
  endrule

  method Action start(Bit#(32) a, Bit#(32) b) × if (!busy_flag);
    x <= a; y <= b; busy_flag <= True;
  endmethod

  method ActionValue#(Bit#(32)) getResult × if (busy_flag&&(x==0));
    busy_flag <= False; return y;
  endmethod
endmodule
```

Assume b != 0

Guard?

```
interface GCD;
  method Action start (Bit#(32) a, Bit#(32) b);
  method ActionValue#(Bit#(32)) getResult;
endinterface
```

Rules with guards

- Like a method, a rule can also have a guard

```
rule foo if (p); — guard
  begin x1 <= e1; x2 <= e2; end
endrule
```


Syntax: In rules,
"if" is optional
before the guard!

- A rule can execute only if it's guard is true, i.e., if the guard is false the rule has no effect
- True guards can be omitted. Equivalently, the absence of a guard means the guard is always true
- An alternative way to write the gcd rule:

```
rule gcdSubtract if (x >= y);
  x <= x - y;
endrule
rule gcdSwap if !(x >= y) && (x != 0);
  x <= y; y <= x;
endrule
```

Rule
splitting

Streaming a module

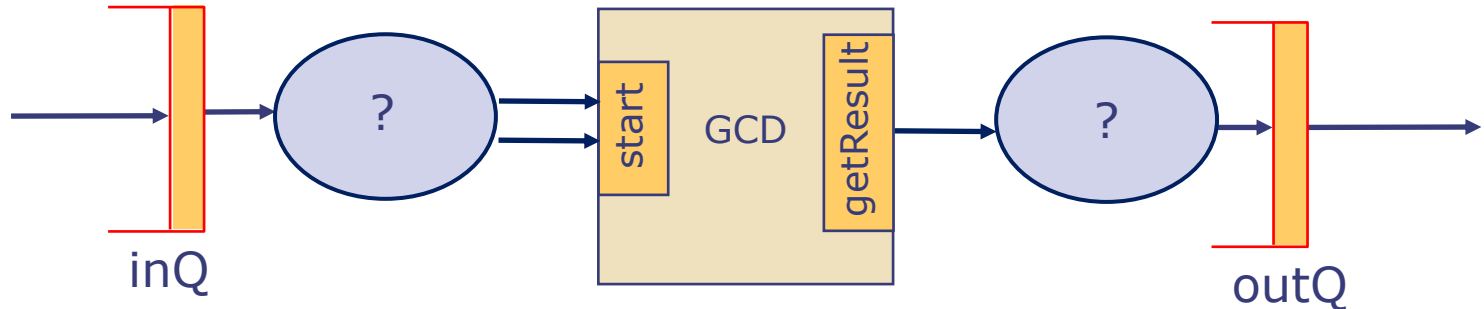


- Suppose we have a queue of pairs of numbers and we want to compute their GCDs and put the results in an output queue
- We can build such a system by creating the following modules

```
Fifo#(1,Vector#(2,t)) inQ <- mkFifo;  
Fifo#(1,t) outQ <- mkFifo;  
GCD gcd <- mkGCD;
```

- To glue these modules together we define two rules:
 - `invokeGCD` to push data from `inQ` into `gcd`
 - `getResult` to fetch result from `gcd` and put it into `outQ`

Streaming a module: code

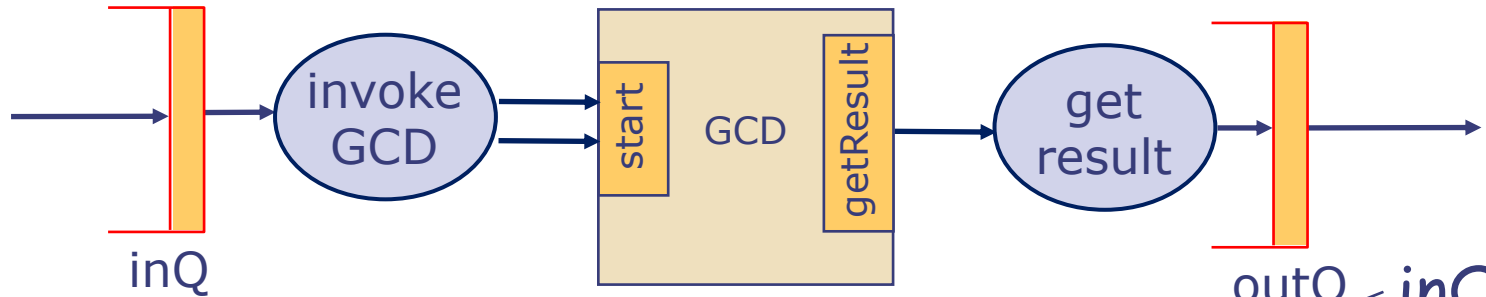

rule invokeGCD ~~X~~ if(inQ.first.rdy && inQ.deq.rdy && gcd.start.rdy);
let x = inQ.first[0];
let y = inQ.first[1];
gcd.start(x,y);
inQ.deq;
endrule

inQ is not empty

gcd is not busy


rule getResult ~~X~~ if(gcd.getResult.rdy && outQ.enq.rdy);
let x <- gcd.getResult;
outQ.enq(x);
endrule

Action value method

Implicit guards?

Power of Abstraction:

Another GCD implementation

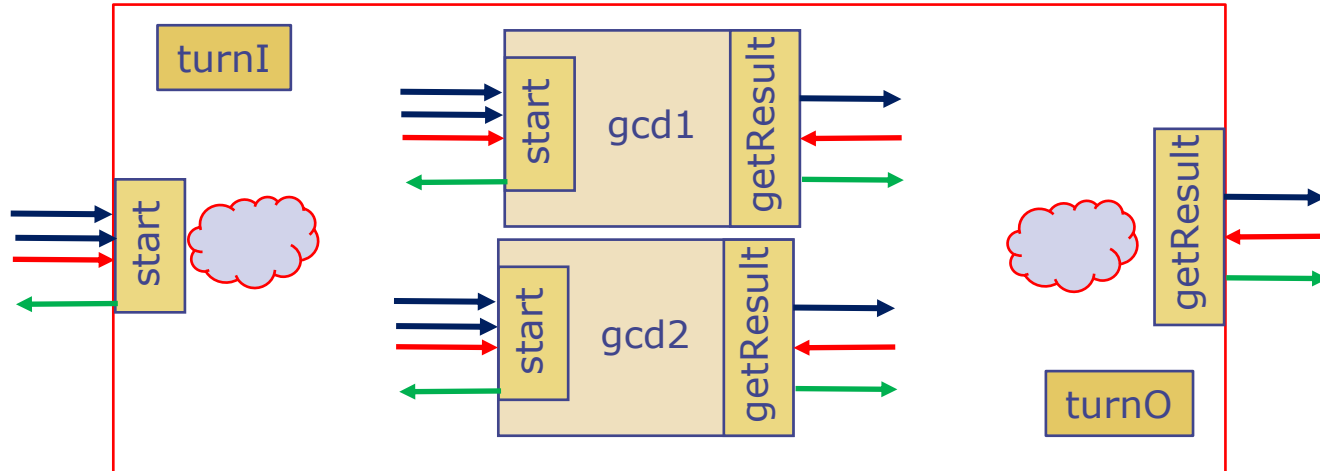

- A GCD module with the same interface but with twice the throughput; uses two gcd modules in parallel
- turnI is used by the start method to direct the input to the gcd whose turn it is and then turnI is flipped
- Similarly, turnO is used by getResult to get the output from the appropriate gcd, and then turnO is flipped

```
interface GCD;  
    method Action start (Bit#(32) a, Bit#(32) b);  
    method ActionValue#(Bit#(32)) getResult;  
endinterface
```

High-throughput GCD code

```
module mkMultiGCD (GCD);
```

```
  GCD gcd1 <- mkGCD();
```

```
  GCD gcd2 <- mkGCD();
```

```
  Reg#(Bool) turnI <- mkReg(False);
```

```
  Reg#(Bool) turnO <- mkReg(False);
```

```
  method Action start(Bit#(32) a, Bit#(32) b);
```

```
    if (turnI) gcd1.start(a,b); else gcd2.start(a,b);
```

```
    turnI <= !turnI;
```

```
  endmethod
```

```
  method ActionValue (Bit#(32)) getResult;
```

```
    Bit#(32) y;
```

```
    if (turnO) y <- gcd1.getResult
```


```
    else y <- gcd2.getResult;
```

```
    turnO <= !turnO
```

```
    return y;
```

```
  endmethod
```

```
endmodule
```

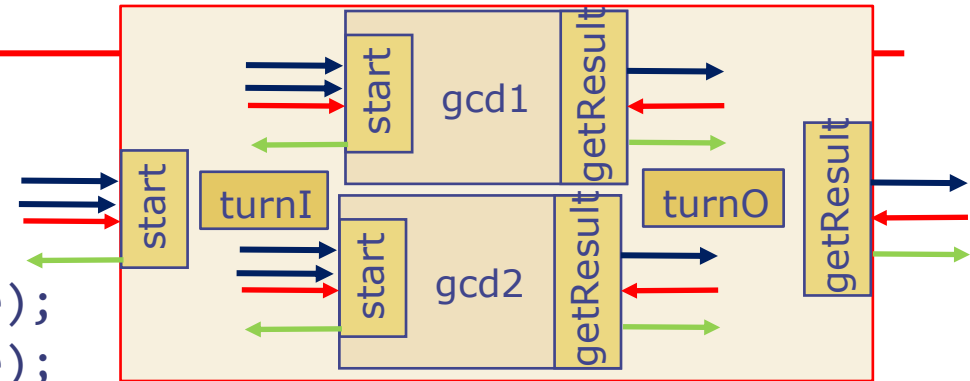

```
interface GCD;
```

```
  method Action start (Bit#(32) a, Bit#(32) b);
```

```
  method ActionValue#(Bit#(32)) getResult;
```

```
endinterface
```

Summary

- Modules with guarded interfaces is a new way of expressing sequential circuits
- A module, like an object in OO languages, has a well-defined interface
- However, unlike software OO languages, the interface methods are *guarded*; it can be applied only if it is “ready”
- The compiler ensures that a method is enabled only when it is ready
- The modules are glued together (composed) using *atomic actions*, which call methods
- An atomic action can execute only if all the called methods can be executed simultaneously

next lecture - Hardware synthesis

Take-home problem

What is the difference in the behavior of these two implementations of enq? Are they both correct?

```
// guarded  
method Action enq(t x) if (!v) ;  
    v <= True; d <= x;  
endmethod
```

versus

```
//conditional  
method Action enq(t x);  
    if (!v) begin v <= True; d <= x; end  
endmethod
```