

# Design Tradeoffs in Arithmetic Circuits


*Arvind*

Computer Science & Artificial Intelligence Lab  
M.I.T.

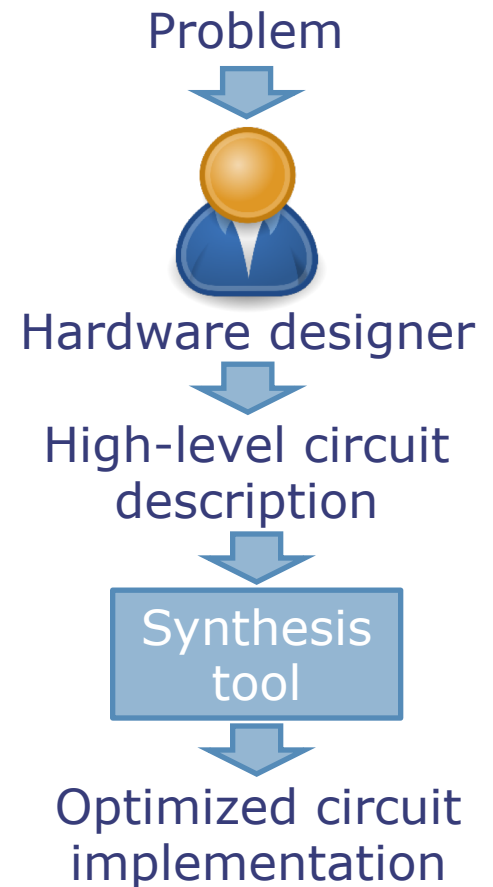
# Algorithmic Tradeoffs in Hardware Design

---

- Each function allows many implementations with widely different delay, area, and power tradeoffs
- Choosing the right **algorithms** is key to optimizing your design
  - Tools cannot compensate for an inefficient algorithm (in most cases)
  - Just like programming software
- Case study: Building a better adder



# Ripple-Carry Adder: Simple but Slow

 

- Worst-case path: Carry propagation from LSB to MSB, e.g., when adding  $11\dots111$  to  $00\dots001$

$$t_{PD} = (n-1) * t_{PD, CI \rightarrow CO} + t_{PD, CI \rightarrow S} \approx \Theta(n)$$

- $\Theta(n)$  is read “order  $n$ ” and tells us that the latency of our adder grows **linearly** with the number of bits of the operands

# Asymptotic Analysis

---

- Suppose some computation takes  $n^2+2n+3$  steps
- We say it takes  $\Theta(n^2)$  (read “is of order  $n^2$ ”) steps
- Why?

because  $2n^2 > n^2+2n+3 > n^2$

except for a few small integers (1,2 and 3)

- Formally,  $g(n)=\Theta(f(n))$  iff there exist  $C_2 \geq C_1 > 0$  such that for all but *finitely many* integers  $n \geq 0$ ,


$$C_2 \cdot f(n) \geq g(n) \geq C_1 \cdot f(n)$$



$g(n) = O(f(n))$

$\Theta(\dots)$  implies both inequalities;  
 $O(\dots)$  implies only the first.
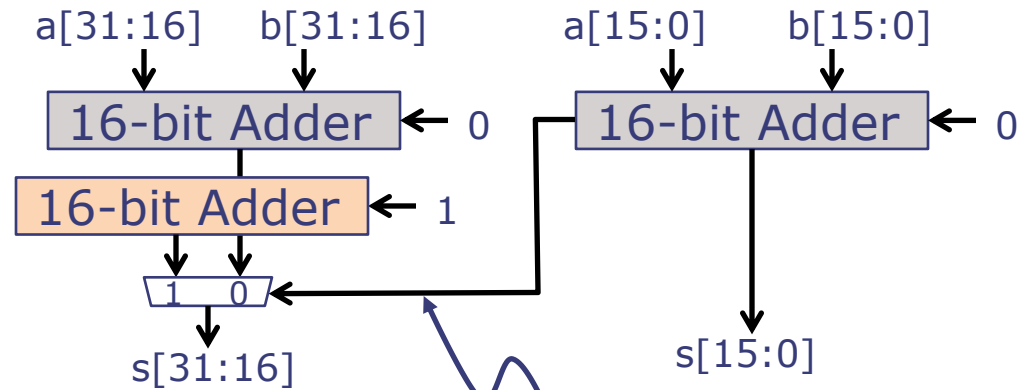
# Carry-Select Adder Trades Area for Speed




The carry-out of the low half selects the correct version of the high-half addition.

- Propagation delay:  $t_{PD,32} = t_{PD,16} + t_{PD,MUX}$ 
  - If we used 16-bit ripple-carry adders, this would roughly halve delay over a 32-bit ripple-carry adder

*Drawbacks? Consumes much more area than ripple-carry adder  
Wide mux adds significant delay*
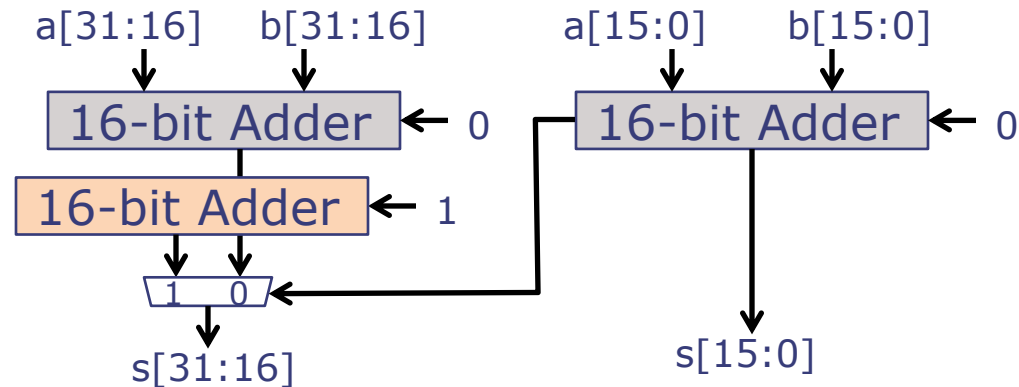
# Carry-Select Adder Trades Area for Speed



```
function Bit#(33) csa32(Bit#(32) a, Bit#(32) b, Bit#(1) c);  
  let csL = add16(a[15:0], b[15:0], c);  
  let csU = (csL[16] == 0) ? add16(a[31:16], b[31:16], 0)  
    : add16(a[31:16], b[31:16], 1);  
  return {csU, csL[15:0]};  
endfunction
```

We can use any type of adder, including CSA

# Recursive Carry-Select Adder

---

- It is easier to write the code than to draw a picture

```
function Bit#(33) csa32(Bit#(32) a, Bit#(32) b, Bit#(1) c);  
  let csL = csa16(a[15:0], b[15:0], c);  
  let csU = (csL[16] == 0) ? csa16(a[31:16], b[31:16], 0)  
                    : csa16(a[31:16], b[31:16], 1);  
  return {csU,csL[15:0]};  
endfunction
```

// following functions can be defined similarly

```
function Bit#(17) csa16(Bit#(16) a, Bit#(16) b, Bit#(1) c);  
function Bit#(9)  csa8 (Bit#(8)  a, Bit#(8)  b, Bit#(1) c);  
function Bit#(5)  csa4 (Bit#(4)  a, Bit#(4)  b, Bit#(1) c);  
function Bit#(3)  csa2 (Bit#(2)  a, Bit#(2)  b, Bit#(1) c);  
// let csa2 use fa instead of csa1
```

# CSA analysis

---


- Carry delay  $t_{PD,n} = \Theta(\log n)$  but lots of extra hardware
- Area calculation
  - $csa32 = 3 csa16 + mux17$
  - $csa16 = 3 csa8 + mux9$
  - $csa8 = 3 csa4 + mux5$
  - $csa4 = 3 csa2 + mux3$
  - $csa2 = 3 fa + mux2$
  - $fa = 5 \text{ gates}$
  - $muxn = 3n+1 \text{ gates}$
- Total gates in csa32
  - $243 fa + 81 mux2 + 27 mux3 + 9 mux5 + 3 mux9 + mux17$
  - $= 2339 \text{ gates}$
- Lots of circuits are duplicated but Boolean optimizations by the compiler may reduce the size of the circuit
  - Many of the 243 fa's have the same inputs

32-RCA has an area of 32 fa  
 $= 32 \times 5 = 160 \text{ gates}$

Wait until the end for some  
synthesis results




# Carry-Lookahead Adders (CLAs)

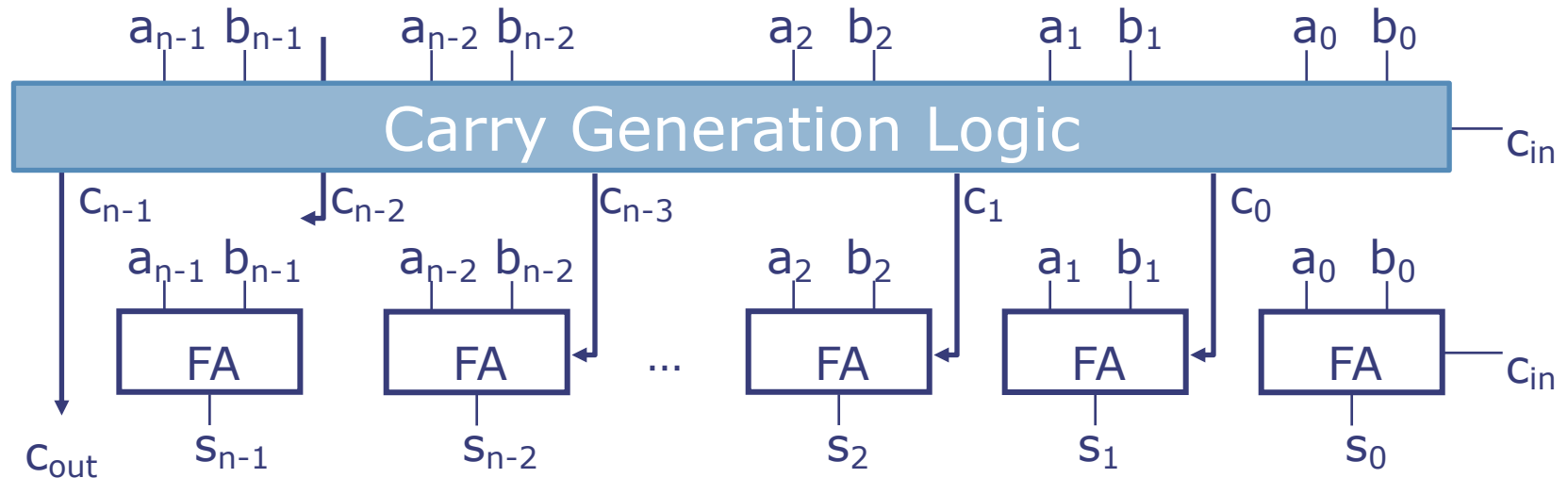

- CLAs compute all carry bits in  $\Theta(\log n)$  delay
- Key idea: Transform chain of carry computations into a tree
  - Transforming a chain of associative operations (e.g., AND, OR, XOR) into a tree is easy
  - But how to do this with carries?

# Full Adder

A	B	C <sub>in</sub>	S	C <sub>out</sub>
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Boolean equations

$$s = (\sim a \cdot \sim b \cdot c_{in}) + (\sim a \cdot b \cdot \sim c_{in}) + (a \cdot \sim b \cdot \sim c_{in}) + (a \cdot b \cdot c_{in})$$

$$c_{out} = (\sim a \cdot b \cdot c_{in}) + (a \cdot \sim b \cdot c_{in}) + (a \cdot b \cdot \sim c_{in}) + (a \cdot b \cdot c_{in})$$

Optimized

$$t = a \oplus b$$

$$s = t \oplus c_{in}$$

$$c_{out} = t \cdot c_{in} + a \cdot b$$

# Full Adder: Optimization steps

---

$$\begin{aligned}s &= (\sim a \cdot \sim b \cdot c_{in}) + (\sim a \cdot b \cdot \sim c_{in}) + (a \cdot \sim b \cdot \sim c_{in}) + (a \cdot b \cdot c_{in}) \\&= (\sim a \cdot \sim b + a \cdot b) \cdot c_{in} + (\sim a \cdot b + a \cdot \sim b) \cdot \sim c_{in} \\&= \sim(a \oplus b) \cdot c_{in} + (a \oplus b) \cdot \sim c_{in} \\&= a \oplus b \oplus c_{in}\end{aligned}$$

$$\begin{aligned}c_{out} &= (\sim a \cdot b \cdot c_{in}) + (a \cdot \sim b \cdot c_{in}) + (a \cdot b \cdot \sim c_{in}) + (a \cdot b \cdot c_{in}) \\&= (a \oplus b) \cdot c_{in} + a \cdot b\end{aligned}$$

$$c_{out} = (a+b) \cdot c_{in} + a \cdot b$$

This is also correct

Sharing common sub-expressions

$$t = a \oplus b$$

$$s = t \oplus c_{in}$$


$$c_{out} = t \cdot c_{in} + a \cdot b$$

# Carry Generation and Propagation

---

$$C_{out} = a \cdot b + (a \oplus b) \cdot C_{in}$$

 generates a carry      propagates a carry




$$C_{out} = g + p \cdot C_{in}$$

where  $g = a \cdot b$  and  $p = a \oplus b$

- $g=1 \rightarrow C_{out} = 1$  (FA generates a carry)
- $p=1$  (and  $g=0$ )  $\rightarrow C_{out} = C_{in}$  (FA propagates carry)


Notice  $p$  and  $g$  don't depend upon  $C_{in}$
 
# Generate and Propagate compose hierarchically




$$C_{out} = g + p \cdot C_{in}$$
 
$$\text{where } g = a \cdot b \text{ and } p = a \oplus b$$


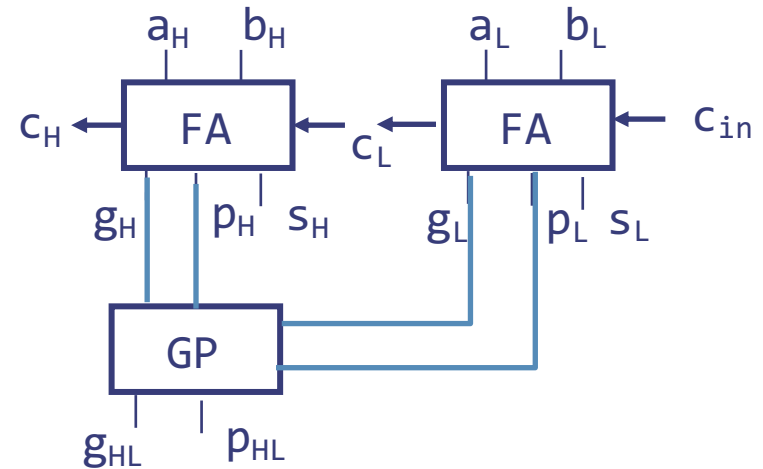
$$\begin{aligned} C_H &= g_H + p_H \cdot C_L \\ &= g_H + p_H \cdot (g_L + p_L \cdot C_{in}) \\ &= \underbrace{g_H + p_H \cdot g_L}_{g_{HL}} + \underbrace{p_H \cdot p_L}_{p_{HL}} \cdot C_{in} \end{aligned}$$




$$g_{HL} = g_H + p_H \cdot g_L$$

$$p_{HL} = p_H \cdot p_L$$

 
# CLA Building Blocks

---


- Step 1: Generate individual  $g$  &  $p$  signals



 - Step 2: Combine adjacent  $g$  &  $p$  signals




- Step 3: Generate individual carries

 

There are many CLA variants. Let's derive the Brent-Kung CLA.


# Generating and Combining gp's

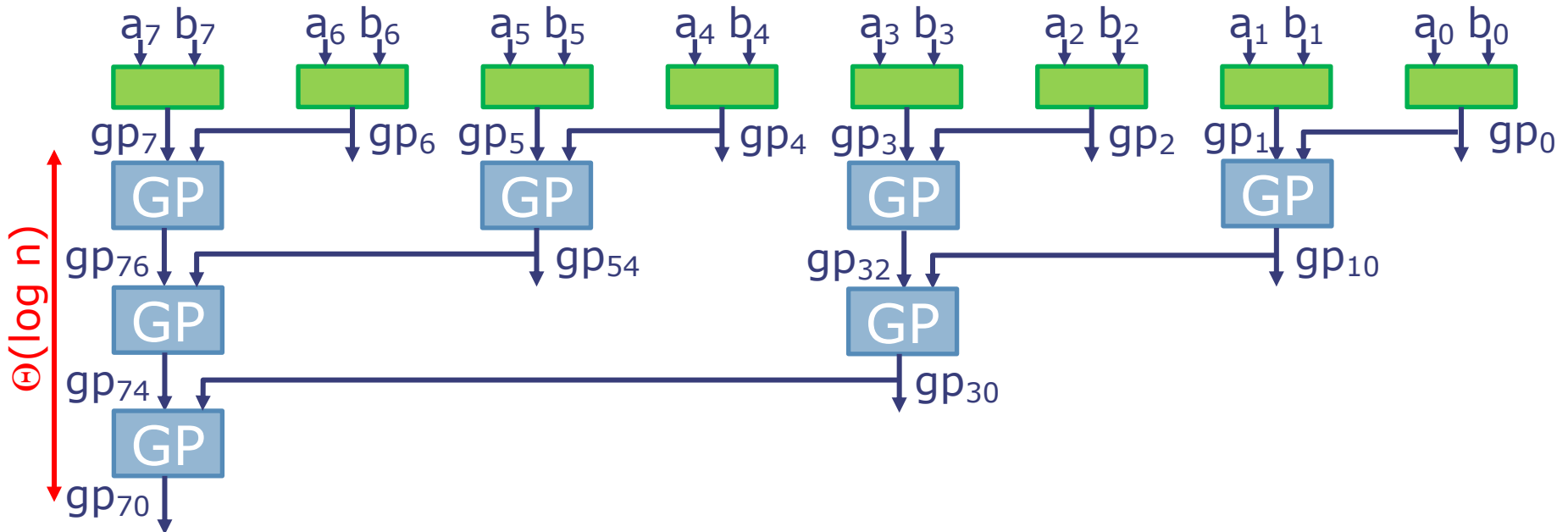

*How does delay grow  
with number of bits?*

$\Theta(\log n)$

# Generating the Carries

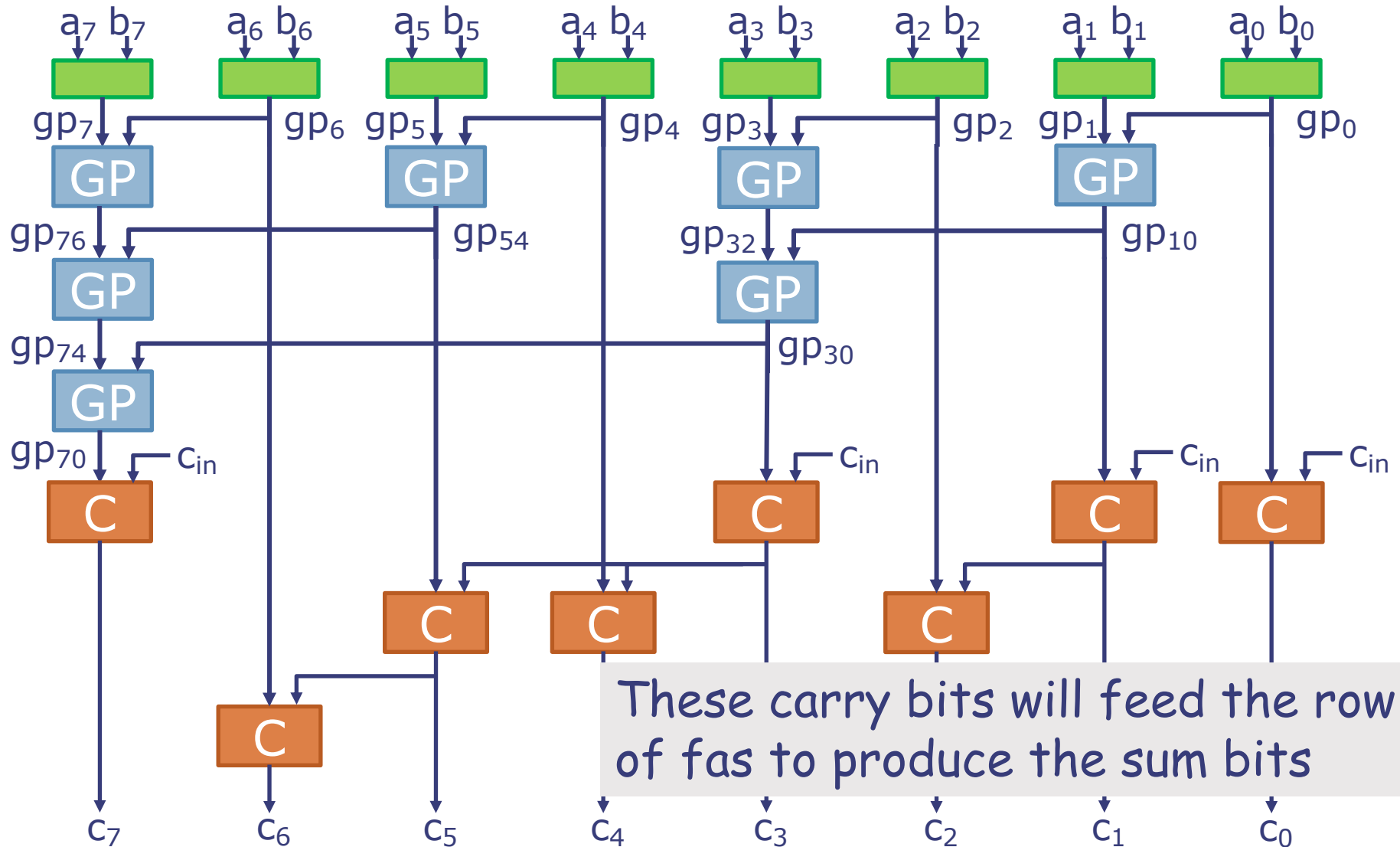



# Carry-Lookahead Adder Takeaways

---

- There are many CLA designs
  - We've seen a Brent-Kung CLA
  - Several other types (e.g., Kogge-Stone)
  - Different variants for each type, e.g., using higher-radix trees to reduce depth
- This technique is useful beyond adders: computes any one-dimensional binary recurrence in  $\Theta(\log n)$  delay
  - e.g., comparators, priority encoders, etc.

# Some Synthesis Results

## Brian Wheatman

	Time Opt Basic gates	Time Opt Ext gates	Space Opt Basic gates	Space Opt Ext gates
Ripple-Carry Adder (RCA)				
Gates	413	164	414	158
Area ( $\mu\text{m}^2$ )	295	180	296	177
Delay (ps)	742	680	758	690
Recursive Carry-Select Adder				
Gates	970	663	840	564
Area ( $\mu\text{m}^2$ )	727	604	630	519
Delay (ps)	226	233	340	302
Kogge-Stone Adder				
Gates	963	530	905	498
Area ( $\mu\text{m}^2$ )	697	483	639	464
Delay (ps)	175	167	182	201

# Summary

---

- Choosing the right algorithms is crucial to design good digital circuits—tools can only do so much!
- Carry-lookahead adders perform  $\Theta(\log n)$  addition with some area cost. This technique can be used to optimize a broad class of circuits.