

6.004 Recitation Problems
L13 – RISC-V Processor

Single-Cycle RISC-V Processor

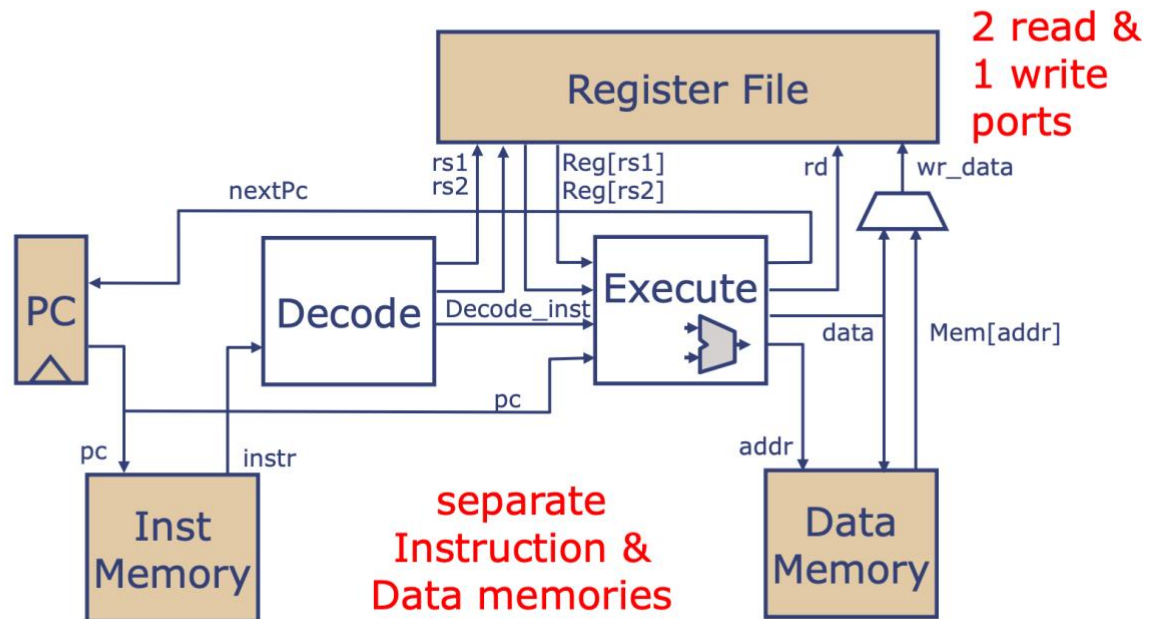


Diagram 1: Abstract Version

- Contains all major components: PC Register, Instruction and Data memories, Decode logic, Execute logic (including the ALU), and Register file
- Skips some details in the wiring of signals to increase readability

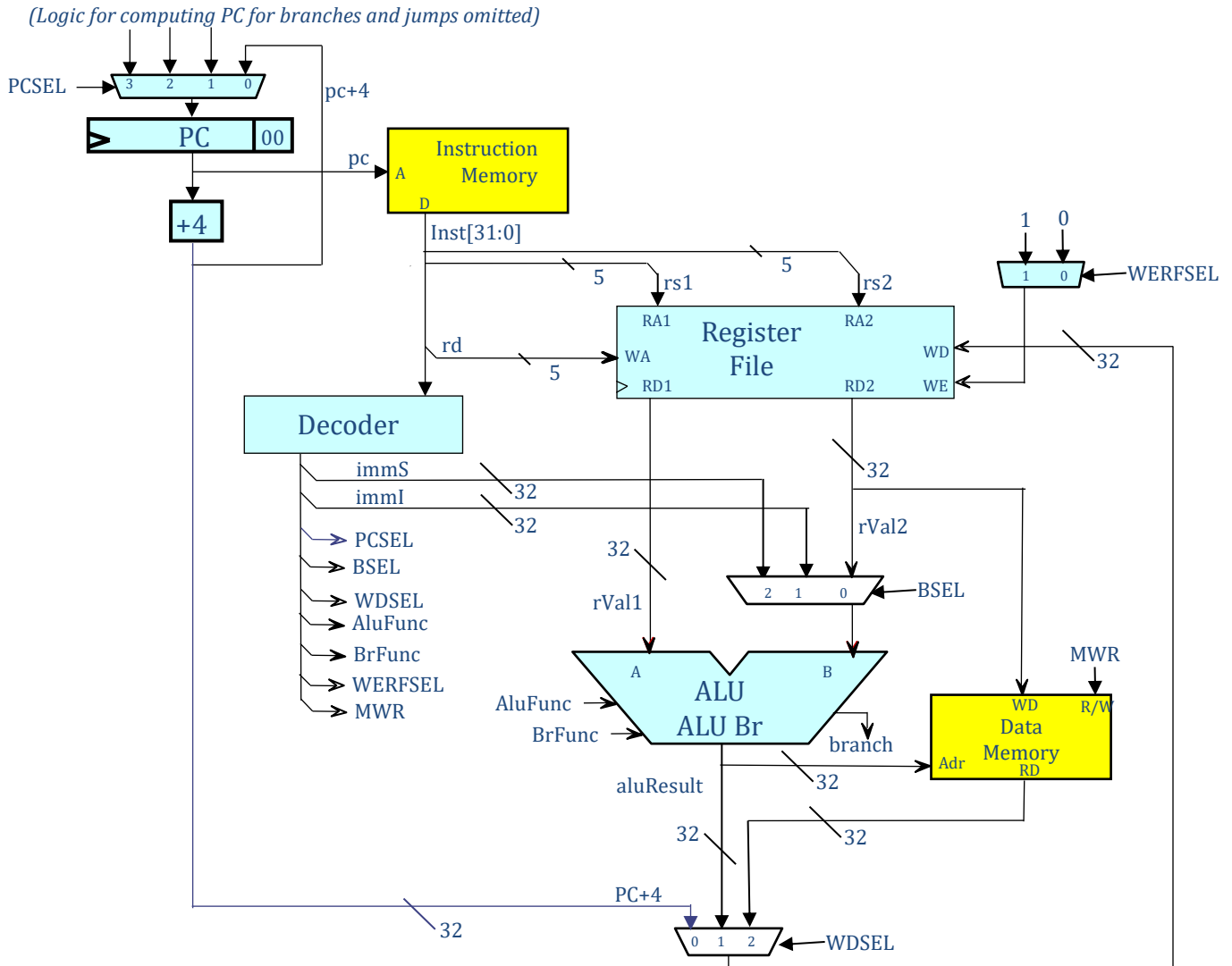


Diagram 2: Detailed Version

- Also contains all of the major components, as well as additional details like muxes on inputs, descriptions of various signal contents and bit widths
- Both diagrams are equivalent! Differ only in level of detail

RISC-V Processor: Components

Refer to the 6.004 ISA Reference Tables (Website > Resources) for details about each instruction.

ProcTypes

```
typedef Bit#(32) Word;
```

```
// Branch function enumeration
```

```
typedef enum {
```

```
    Eq,
```

```
    Neq,
```

```
    Lt,
```

```
    Ltu,
```

```
    Ge,
```

```
    Geu,
```

```
    Dbr
```

```
} BrFunc;
```

```
typedef enum {
```

```
    OP,
```

```
    OPIMM,
```

```
    BRANCH,
```

```
    LUI,
```

```
    JAL,
```

```
    JALR,
```

```
    LOAD,
```

```
    STORE,
```

```
    AUIPC,
```

```
    Unsupported
```

```
} IType;
```

```
// Return type for decode()
```

```
typedef struct {
```

```
    IType iType;
```

```
    AluFunc aluFunc;
```

```
    BrFunc brFunc;
```

```
    Maybe#(RIndx) dst;
```

```
    RIndx src1;
```

```
    RIndx src2;
```

```
    Word imm;
```

```
} DecodedInst;
```

```
// Register Index Type
```

```
typedef Bit#(5) RIndx;
```

```
// Register File writes
```

```
typedef struct {
```

```
    RIndx index;
```

```
    Word data;
```

```
} RegWriteArgs;
```

```
// Return type for execute()
```

```
typedef struct {
```

```
    IType iType;
```

```
    Maybe#(RIndx) dst;
```

```
    Word data;
```

```
    Word addr;
```

```
    Word nextPc;
```

```
} ExecInst;
```

```
// Memory writes
```

```
typedef struct {
```

```
    Word addr;
```

```
    Word data;
```

```
} MemWriteReq;
```

```

// Opcode
Bit#(7) opOpImm  = 7'b0010011;
Bit#(7) opOp     = 7'b0110011;
Bit#(7) opLui    = 7'b0110111;
Bit#(7) opJal    = 7'b1101111;
Bit#(7) opJalr   = 7'b1100111;
Bit#(7) opBranch = 7'b1100011;
Bit#(7) opLoad   = 7'b0000011;
Bit#(7) opStore  = 7'b0100011;
Bit#(7) opAuipc  = 7'b0010111;

// funct3 - ALU
Bit#(3) fnADD    = 3'b000;
Bit#(3) fnSLL    = 3'b001;
Bit#(3) fnSLT    = 3'b010;
Bit#(3) fnSLTU   = 3'b011;
Bit#(3) fnXOR    = 3'b100;
Bit#(3) fnSR     = 3'b101;
Bit#(3) fnOR     = 3'b110;
Bit#(3) fnAND    = 3'b111;

// funct3 - Branch
Bit#(3) fnBEQ    = 3'b000;
Bit#(3) fnBNE    = 3'b001;
Bit#(3) fnBLT    = 3'b100;
Bit#(3) fnBGE    = 3'b101;
Bit#(3) fnBLTU   = 3'b110;
Bit#(3) fnBGEU   = 3'b111;

// funct3 - Load
Bit#(3) fnLW     = 3'b010;
Bit#(3) fnLB     = 3'b000;
Bit#(3) fnLH     = 3'b001;
Bit#(3) fnLBU    = 3'b100;
Bit#(3) fnLHU    = 3'b101;

// funct3 - Store
Bit#(3) fnSW     = 3'b010;
Bit#(3) fnSB     = 3'b000;
Bit#(3) fnSH     = 3'b001;

// funct3 - JALR
Bit#(3) fnJALR   = 3'b000;

```

Register File

```

module RegisterFile;
    Vector#(32, Reg#(Word)) regs(0);

    method Word rd1(RIndx rindx) = regs[rindx];
    method Word rd2(RIndx rindx) = regs[rindx];

    input Maybe#(RegWriteArgs) wr default = Invalid;

    rule rfWrite;
        if (isValid(wr)) begin
            RegWriteArgs rwd = fromMaybe(?, wr);
            if (rwd.index != 0)
                regs[rwd.index] <= rwd.data;
        end
    endrule
endmodule

```

Decode

```
function DecodedInst decode(Bit#(32) inst);
    let opcode = inst[6:0];
    let funct3 = inst[14:12];
    let funct7 = inst[31:25];
    let dst     = inst[11:7];
    let src1    = inst[19:15];
    let src2    = inst[24:20];

    Maybe#(RIndx) validDst = Valid(dst);
    Maybe#(RIndx) dDst = Invalid; // default value
    RIndx dSrc = 5'b0;

    // DEFAULT VALUES - Use the following for your default values:
    // dst: dDst, src1: dSrc, src2: dSrc, imm: immD, BrFunc: Dbr, AluFunc: ?

    // We have provided a default value and done immB for you.
    Word immD32 = signExtend(1'b0); // default value
    Bit#(12) immB = { inst[31], inst[7], inst[30:25], inst[11:8] };
    Word immB32 = signExtend({immB, 1'b0});
    Bit#(20) immU = 0; // TODO
    Word immU32 = 0; // TODO
    Bit#(12) immI = 0; // TODO
    Word immI32 = 0; // TODO
    Bit#(20) immJ = 0; // TODO
    Word immJ32 = 0; // TODO
    Bit#(12) immS = 0; // TODO
    Word immS32 = 0; // TODO

    DecodedInst dInst = unpack(0);
    dInst.iType = Unsupported; // unsupported by default

    case (opcode)
        opAuipc: begin
            dInst = DecodedInst {
                iType: AUIPC,
                dst: validDst,
                src1: dSrc,
                src2: dSrc,
                imm: immU32,
                brFunc: Dbr,
                aluFunc: ?
            };
        end
        opLui: // TODO
```

Decode (continued)

```
    opOpImm: begin
        dInst.iType = OPIMM;
        dInst.src1  = src1;
        dInst.imm   = immI32;
        dInst.dst   = validDst;

        case (funct3)
            fnAND : dInst.aluFunc = And; // Decode ANDI instructions
            fnOR  : dInst.iType = Unsupported; // TODO
            fnXOR : dInst.iType = Unsupported; // TODO
            fnADD : dInst.iType = Unsupported; // TODO
            fnSLT : dInst.iType = Unsupported; // TODO
            fnSLTU: dInst.iType = Unsupported; // TODO
            fnSLL : case (funct7)
                7'b0000000: dInst.aluFunc = Sll;
                // Otherwise we must say the instruction is invalid:
                default:    dInst.iType = Unsupported;
            endcase
            fnSR  : // TODO
                dInst.iType = Unsupported;
                default: dInst.iType = Unsupported;
        endcase
    end
    opOp: // TODO
    opBranch: // TODO
    opJal: // TODO
    opLoad: // TODO
    opStore: // TODO
    opJalr: // TODO
endcase
return dInst;
endfunction
```

Branch ALU (Execute.ms)

```
function Bool aluBr(Word a, Word b, BrFunc brFunc);
  Bool res = case (brFunc)
    Eq:      (a == b);
    Neq:     (a != b);
    Lt:      signedLT(a, b);
    Ltu:     (a < b);
    Ge:      signedGE(a, b);
    Geu:     (a >= b);
    default: False;
  endcase;
  return res;
endfunction
```

Execute

```
function ExecInst execute(DecodedInst dInst, Word rVal1, Word rVal2, Word pc);
  let imm = dInst.imm;
  let brFunc = dInst.brFunc;
  let aluFunc = dInst.aluFunc;
  let aluVal2 = dInst.iType == OPIMM ? imm : rVal2;

  Word data = case (dInst.iType)
    AUIPC:    pc + imm;
    LUI:      0; // TODO
    OP, OPIMM: 0; // TODO
    JAL, JALR: 0; // TODO
    STORE:    0; // TODO
    default:  0;
  endcase;

  Word nextPc = case (dInst.iType)
    BRANCH: 0; // TODO Replace 0 with the correct expression
    JAL:    0; // TODO Replace 0 with the correct expression
    JALR: (rVal1 + imm) & ~1; // "& ~1" clears the bottom bit.
    default: pc + 4;
  endcase;

  Word addr = 0; // TODO Replace 0 with the correct expression

  return ExecInst{iType: dInst.iType, dst: dInst.dst, data: data,
                  addr: addr, nextPc: nextPc};
endfunction
```

Magic Memory

```
module MagicMemory;
    // 64 KB magic memory array
    MagicMemoryArray magicMem("mem.vmh");

    method Word read(Word addr) = magicMem.sub(truncate(addr >> 2));

    input Maybe#(MemWriteReq) write default = Invalid;

    rule doWrite;
        if (isValid(write)) begin
            MemWriteReq req = fromMaybe(?, write);
            if (req.addr == 'h4000_0000) begin
                // Write character to stdout
                $write("%c", req.data[7:0]);
            end else if (req.addr == 'h4000_0004) begin
                // Write integer to stdout
                $write("%0d", req.data);
            end else if (req.addr == 'h4000_1000) begin
                // Exit simulation
                if (req.data == 0) begin
                    $display("PASSED");
                end else begin
                    $display("FAILED %0d", req.data);
                end
            end
            $finish;
        end else begin
            // Write memory array
            magicMem.upd = ArrayWriteReq{idx: truncate(req.addr >> 2),
                                         data: req.data};
        end
    end
endrule
endmodule
```


Processor

```
module Processor;
  Reg#(Word) pc(0);
  RegisterFile rf;
  MagicMemory iMem; // Memory for loading instructions
  MagicMemory dMem; // Memory for loading and storing data

  rule doSingleCycle;
    // Load the instruction from instruction memory (iMem)
    Word inst = 0; // TODO

    // Decode the instruction
    DecodedInst dInst = unpack(0); // TODO

    // Read the register values used by the instruction
    Word rVal1 = 0; // TODO
    Word rVal2 = 0; // TODO

    // Compute all outputs of the instruction
    ExecInst eInst = unpack(0); // TODO

    if (eInst.iType == LOAD) begin
      // TODO: Load from data memory (dMem) if needed
    end else if (eInst.iType == STORE) begin
      // TODO: Store to data memory (dMem) if needed
    end

    if (isValid(eInst.dst)) begin
      // TODO: Write to a register if the instruction requires it
    end

    // TODO: Update pc to the next pc
  endrule
endmodule
```

Problem 1.

Decode the following 32-bit RISC-V instructions:

1. 0100000 00001 00100 000 00011 0110011

2. 0100000 00101 00010 101 00111 0010011

Problem 2. ★

The RISC-V LUI instruction, Load Upper Immediate, loads a 20-bit immediate into the upper 20 bits of the specified destination register (and sets the lower 12 bits to zero). What modifications to the datapath are needed to implement the LUI instruction?

Problem 3. ★

We want to add the following instruction to the RISC-V ISA:


```
cmvz rd, rs1, rs2
```

This new **cmvz** instruction is a *conditional move*: it checks the contents of source register **rs1**, and if it's 0, copies the contents of source register **rs2** into **rd**. In other words:

```
if (reg[rs1] == 0) begin
    reg[rd] <= reg[rs2];
end
```

We would like to update the hardware diagram of the single-cycle processor to support this new instruction, reusing the existing **branch ALU** comparison logic to check if **rs1** is 0. In the diagram below, we have added extra inputs to the BSEL and WDESEL, and WERFSEL muxes to support reusing the branch ALU in this way.

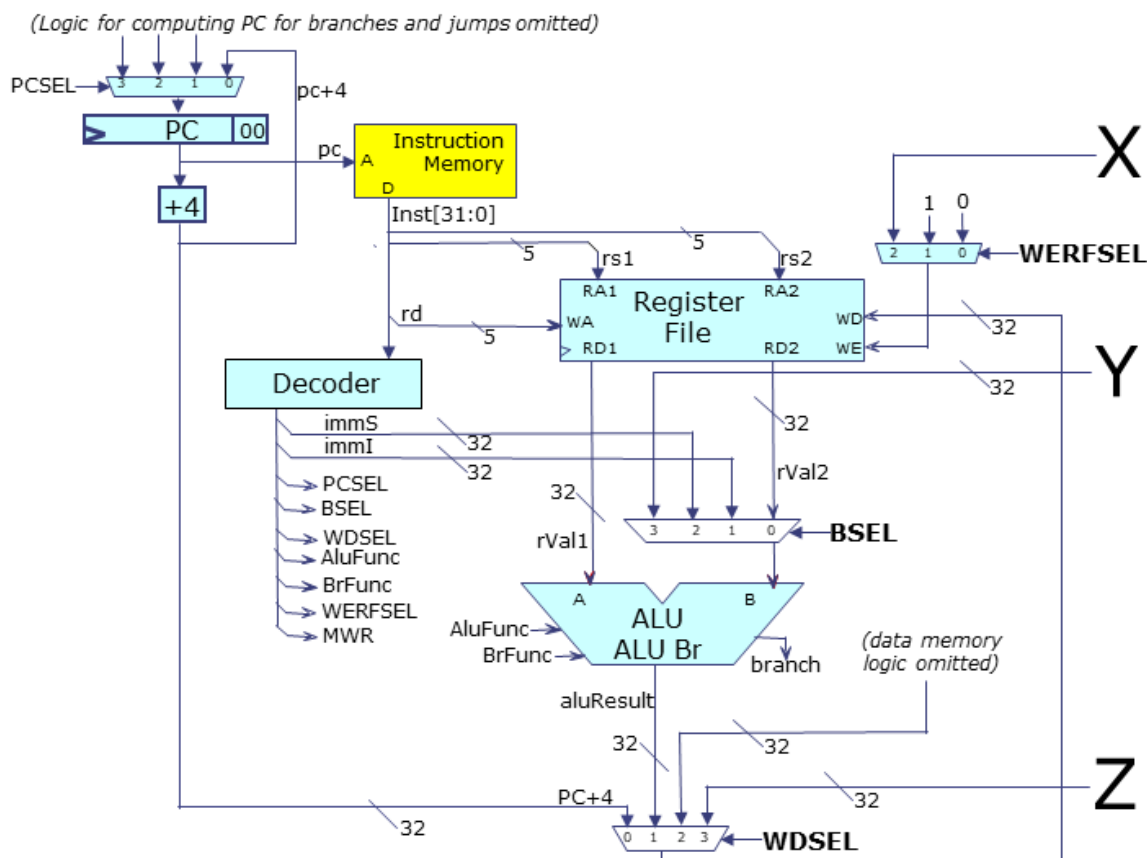Assume that when the decoder decodes CMVZ, it outputs BrFunc = Eq, BSEL = 3, WDESEL = 3, and WERFSEL = 2. It also outputs PCSEL = 0 so that the next value of PC will be PC + 4.



Summary of some of the relevant processor components in the above diagram:

- One register in the register file can be written to each cycle by providing the register index in WA and the data to write in WD. The data is only written if the write enable signal, WE, is 1.
- The ALU receives two inputs, A and B. It computes an arithmetic operation on them specified by AluFunc, outputting the 32-bit result to aluResult, and a comparison specified by BrFunc, outputting the 1-bit result to branch.

- (a) For each of the missing mux inputs X, Y, and Z, write down either a constant or the name of a different wire or port in the processor hardware diagram that should be connected to each input, so that the processor executes CMVZ correctly.

X: _____

Y: _____

Z: _____

- (b) We would like to check that our processor can still decode and execute the old RISC-V instructions correctly. Suppose the processor is decoding an OPIMM instruction, such as ADDI. For each of the select signals we changed (shown in **bold** in the diagram), write down the correct signals that the decoder should produce for such an instruction.

Decoded value of BSEL: _____

Decoded value of WDSEL: _____

Decoded value of WERFSEL: _____

Problem 4.

(a) The RISC-V MUL instruction multiplies two 32-bit values together and places the **lower** 32 bits of the product in the destination register. It has an opcode of 7'b0110011, which is the same as the other OP type instructions, and a funct7 of 7'b0000001, and a funct3 of 3'b000. What changes to the datapath would be needed to support the MUL instruction? Use the combinational multiplier from Lecture 12.

(b) The RISC-V MULH instruction performs the same multiplication in (a), but returns the **upper** 32 bits of the product in the destination register. It has the same opcode and funct7 codes, but its funct3 is 3'b001. What modifications to 3(a) would be needed to support the MULH instruction?

Problem 5. ★

Add a branch if greater-than (BGT) instruction to the provided RISC-V processor. The instruction encoding should match other branch instructions, but have `funct3 = 3'b010`.

Problem 6.

Assume that `aluBr` has been replaced with the new branch ALU function, `newAluBr`, shown below. This new branch ALU is controlled by two control signals: `newBrFunc` and `negate`. When the result of this function is true, the next PC is going to be computed as `pc + imm`.

```
typedef enum {Eq, Lt, Ltu} NewBrFunc;

function Bool newAluBr(Word a, Word b, NewBrFunc newBrFunc, Bool negate);
    Bool res = case (newBrFunc)
        Eq:      (a == b);
        Lt:      signedLT(a, b);
        Ltu:      (a < b);
    endcase;
    return negate ? !res : res;
endfunction
```

- A) Fill in the decoding table below to specify what the control signals should be for each `funct3`. Write an “X” in the table for entries that don’t matter. (Use the ISA [reference card](#) from the course website.)

funct3	newBrFunc	negate
3'b000		
3'b001		
3'b010		
3'b011		
3'b100		
3'b101		
3'b110		
3'b111		