

Combinational Logic and Introduction to Minispec

Reminders:


- Quiz review session tonight 7:30-9:30pm in 6-120
- Lab 2 checkoffs due by tomorrow
- Quiz 1: Thursday 7:30-9:30pm
 - See website or Piazza for room assignments

Lecture Goals

- Learn how to design large combinational circuits through three useful examples:
 - Adder
 - Multiplexers
 - Shifter
- Learn how to implement combinational circuits in the Minispec hardware description language (HDL)
 - Design each combinational circuit as a **function**, which can be simulated or synthesized into gates

Building a Combinational Adder

 - Goal: Build a circuit that takes two n -bit inputs a and b and produces $(n+1)$ -bit output $s = a + b$



- Approach: Implement the binary addition algorithm we have seen (called the standard algorithm)

$$\begin{array}{r} 1110 \text{ — carry} \\ 1110 \\ + 0111 \\ \hline 10101 \end{array}$$

Formalizing the Standard Algorithm

carry —

$$\begin{array}{r} 1110 \\ 1110 \\ + 0111 \\ \hline 10101 \end{array} \quad \rightarrow \quad \begin{array}{r} c_4 c_3 c_2 c_1 0 \\ a_3 a_2 a_1 a_0 \\ + b_3 b_2 b_1 b_0 \\ \hline s_4 s_3 s_2 s_1 s_0 \end{array}$$


- The i^{th} step of each addition
 - Takes three 1-bit inputs: a_i , b_i , c_i (carry-in)
 - Produces two 1-bit outputs: s_i , c_{i+1} (carry-out)
 - The 2-bit output $c_{i+1}s_i$ is the binary sum of the three inputs

Can you build a circuit that performs a single step with what you've learned so far?


Combinational Logic for an Adder

- First, build a full adder (FA), which

 - Adds three one-bit numbers:
 a , b , and carry-in
- Produces a sum bit and a carry-out bit



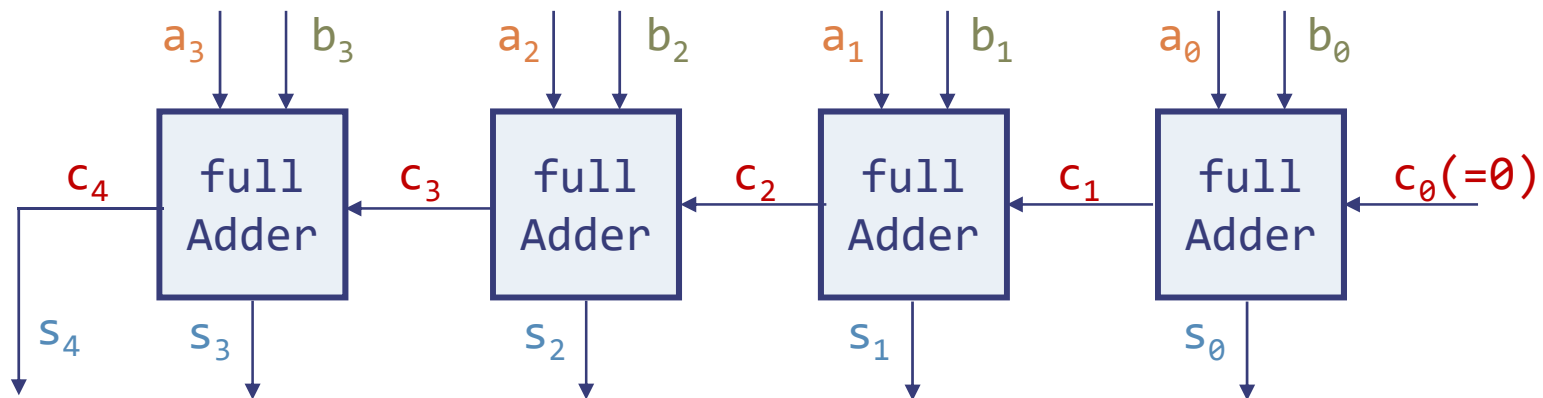- Then, cascade FAs to perform binary addition




- Result: A ripple-carry adder (simple but slow)

Deriving the Full Adder

Truth table

a	b	c _{in}	c _{out}	s
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Boolean expressions

$$s = a \oplus b \oplus c_{in}$$

$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

Describing a 32-bit Adder alternatives

- Truth table with 2^{64} rows and 33 columns
- 32 sets of Boolean equations, where each set describes a FA
- Use some ad-hoc notation to describe recurrences
 - $s_k = a_k \oplus b_k \oplus c_k$
 - $c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k$
$$\left. \begin{array}{l} s_k = a_k \oplus b_k \oplus c_k \\ c_{k+1} = a_k \cdot b_k + a_k \cdot c_k + b_k \cdot c_k \end{array} \right\} 0 \leq k \leq 31$$
- Circuit diagrams: tedious to draw, error-prone
- A hardware description language (HDL), *i.e.*, a programming language specialized to describe hardware
 - Precisely specify the structure and behavior of digital circuits
 - Designs can be automatically simulated or synthesized to hardware
 - Enables building hardware with same principles used to build software (write and compose simple, reusable building blocks)
 - Uses a familiar syntax (functions, variables, control-flow statements, etc.) **But be aware of the differences!**

Introduction to Minispec

A simple HDL based on Bluespec

Combinational Logic as Functions

- In Minispec, combinational circuits are described using functions

Return type Function name Input arguments

```
function Bool inv(Bool x);  
    Bool result = !x;  
    return result;  
endfunction
```

Statement(s),
including a return
statement

- All values have a fixed type, which is known statically (e.g., result is of type Bool)
- Note: Types Start With An Uppercase Letter, variable and function names are lowercase

Bool Type and Operations

- Values of type `Bool` can be `True` or `False`
- `Bool` supports Boolean and comparison operations:

```
Bool a = True;
```

```
Bool b = False;
```

```
Bool x = !a;      // False since a == True
```

```
Bool y = a && b;   // False since b == False
```

```
Bool z = a || b;  // True since a == True
```

```
Bool n = a != b;  // True; equivalent to XOR
```

```
Bool e = a == b;  // False; equivalent to XNOR
```

- `Bool` is the simplest type, but working with many single-bit values is tedious
 - Need a type that represents multi-bit values!

Bit#(n) Type and Operations

- Bit#(n) represents an n-bit value
- Bit#(n) supports the following basic operations:
 - Bitwise logical: \sim (negation), $\&$ (AND), $|$ (OR), \wedge (XOR)

```
Bit#(4) a = 4'b0011; // 4-bit binary 3
Bit#(4) b = 4'b0101; // 4-bit binary 5
Bit#(4) x = ~a;      // 4'b1100
Bit#(4) y = a & b;    // 4'b0001
Bit#(4) z = a ^ b;    // 4'b0110
```


- Bit selection

```
Bit#(1) l = a[0];    // 1'b1 (least significant)
Bit#(3) m = a[3:1];  // 3'b001
```

- Concatenation

```
Bit#(8) c = {a, b}; // 8'b00110101
```


Full Adder in Minispec

 

$$s = a \oplus b \oplus c_{in}$$
$$c_{out} = a \cdot b + a \cdot c_{in} + b \cdot c_{in}$$

```
function Bit#(2) fullAdder(Bit#(1) a, Bit#(1) b, Bit#(1) cin);  
  Bit#(1) s = a ^ b ^ cin;  
  Bit#(1) cout = (a & b) | (a & cin) | (b & cin);  
  return {cout, s};  
endfunction
```


2-bit Ripple-Carry Adder

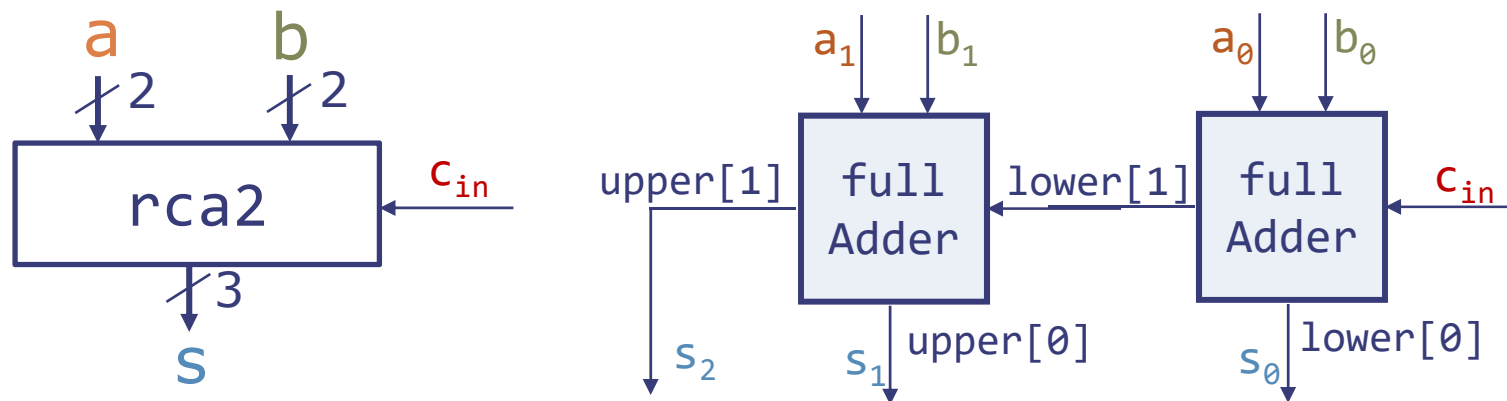

```
function Bit#(3) rca2(Bit#(2) a, Bit#(2) b, Bit#(1) cin);  
    Bit#(2) lower = fullAdder(a[0], b[0], cin);  
    Bit#(2) upper = fullAdder(a[1], b[1], lower[1]);  
    return {upper, lower[0]};  
endfunction
```

- Functions are **inlined**: Each function call creates a new instance (copy) of the called circuit
 - Allows composing simple circuits to build larger ones

4-bit Ripple-Carry Adder

 


```
function Bit#(5) rca4(Bit#(4) a, Bit#(4) b, Bit#(1) cin);  
    Bit#(3) lower = rca2(a[1:0], b[1:0], cin);  
    Bit#(3) upper = rca2(a[3:2], b[3:2], lower[2]);  
    return {upper, lower[1:0]};  
endfunction
```

- Composing functions lets us build larger circuits, but writing very large circuits this way is tedious
 - Next lecture: Writing an n-bit adder in a single function

Multiplexers


2-way Multiplexer

 - A 2-way multiplexer or mux selects between two inputs a and b based on a single-bit input s (select input)





- Gate-level implementation:

 - If a and b are n -bit wide then this structure is replicated n times; s is the same input for all the replicated structures




4-way Multiplexer

  - A 4-way multiplexer selects between four inputs based on the value of a 2-bit input s
 - Typically implemented using 2-way multiplexers
- An n -way multiplexer can be implemented with a tree of $n-1$ 2-way multiplexers



Multiplexers in Minispec

- 2-way mux → Conditional operator

 

Minispec


```
s? b : a
```

Python

```
b if s else a
```

s has type **Bool**; True is treated as 1 and False as 0

- N-way mux → Case expression

 

Minispec



```
case (s)
  0 : a;
  1 : b;
  2 : c;
  3 : d;
endcase
```

s has type **Bit#(2)**

Selecting a Wire: $x[i]$



assume x is 4 bits wide

- Constant selector: e.g., $x[2]$

  

no hardware;
 $x[2]$ is just
the name of
a wire


- Dynamic selector: $x[i]$

  


4-way
mux

Shift operators

Fixed-size shifts

 


 - Fixed size shift operation is cheap in hardware
 - Just wire the circuit appropriately
- Arithmetic shifts are similar



Logical right shift by n

 - Suppose we want a shifter that right-shifts an N -bit input x by n , where $N=32$ and $0 \leq n \leq 31$
- Naïve approach: Create 32 different fixed-size shifters and select using a mux



How many 2-way one-bit muxes are needed to implement this structure?

$$(32-1) * 32 = 992 \\ = \sim 4k \text{ gates}$$

We can do better!


Barrel Shifter

An efficient circuit to perform variable-size shifts

- A barrel shifter performs shift by n using a series of fixed-size power-of-2 shifts
 - For example, shift by 5 ($=4+1$) can be done with shifts of sizes 4 and 1
 - The bit encoding of n tells us which shifts are needed: if the i^{th} bit of n is 1, then we need to shift by 2^i
 - Ex: $5 = 0b00101$
 - Implementation: A cascade of $\log_2 N$ muxes that choose between shifting by 2^i and not shifting


How many 2-way 1-bit muxes?

$$N * \log_2 N = 32 * 5 = 160$$

 

Barrel shifter implementation

 - Example in Minispec for N=4
 - Only need 2 bits for n, why?
- Use conditional operator for 2-way muxes
- Use concatenation and bit selection for fixed shifts



```
function Bit#(4) barrelShifter(Bit#(4) x, Bit#(2) n);  
    Bit#(4) r1 = (n[1] == 0) ? x : {2'b00, x[3:2]};  
    Bit#(4) r0 = (n[0] == 0) ? r1 : {1'b0, r1[3:1]};  
    return r0;  
endfunction
```


Thank you!

Next lecture:
Complex combinational circuits
and advanced Minispec