

Recitation R9

L09 - Sequential Circuits Worksheet

Before looking at the problems, let's look at some important vocabulary for this section.

Combinational circuit: a circuit in which we combine different gates in the circuit, such as encoders, decoders, multiplexers, and demultiplexers. Combinational circuits can have n number of inputs and m number of outputs, and have no cycles (feedback) or state elements.

Circuits with feedback: circuits with cycles that can hold state. An example of such is a D Latch circuit.


D Latch: A D latch circuit's output depends on a clock. If the clock is high, the input passes to output. If the clock is low, the latch holds its output. For the D latch, the latch is asynchronous and the outputs can change as soon as the inputs do.



D Flip Flop: a circuit with two stable states which can store one bit of state information. The output changes state by signals applied to one or more control inputs. A flip-flop is edge-triggered and only changes state when a control signal goes from high to low or low to high.



Finite State Machine: a computation model that can be used to simulate sequential logical and model problems in many fields such as math and artificial intelligence. An example of a finite state machine is shown below:

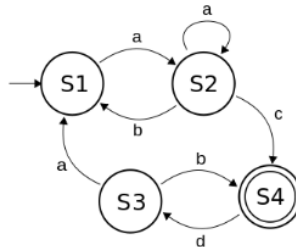

Problem 1

Write the truth tables for both a D latch and a D flip-flop. (Note: Q^* is the next state of Q)

D latch Truth Table

C	D	Q	Q^*

D flip-flop Truth Table

EN	D	Q	Q^*

Problem 2

The following code implements a simple sequential circuit as a module that computes a function over a series of steps. Read the code and answer the questions about it below.

```

interface Foo;
  method Action start(Bit#(32) aIn);
  method ActionValue#(Bit#(32)) getX();
  method Bit#(32) getI();
endinterface

module mkFoo(Foo);
  Reg#(Bit#(32)) a <- mkReg(0);
  Reg#(Bit#(1)) validx <- mkReg(0);
  Reg#(Bit#(32)) x <- mkRegU();
  Reg#(Bit#(32)) i <- mkRegU();

```

```

function Bit#(32) computeB(Bit#(32) in);
    Bit#(32) out = 0;
    if ( in >= 1 ) out = 1;
    if ( in >= 5 ) out = 5;
    if ( in >= 10 ) out = 10;
    return out;
endfunction

rule doComputeStep if (a > 0 && validx == 0);
    let b = computeB(a);
    a <= a - b;
    x <= a;
    validx <= 1;
    i <= i + 1;
endrule

method Action start(Bit#(32) aIn) if (a==0);
    a <= aIn;
    i <= 0;
endmethod

method ActionValue#(Bit#(32)) getX() if (validx == 1);
    validx <= 0;
    return x;
endmethod

method Bit#(32) getI() if (a==0);
    return i;
endmethod
endmodule

```

(A) (4 points) The module using mkFoo is invoking the `getX` method of `mkFoo` at every clock cycle. Remember that an invoked method can only execute when it is ready. If the `start` method is called the first time with `aIn = 28`, what will the output sequence from `getX()`? What is the output of `getI()` after the `start` method is called?

1. Return value sequence of `getX()`:

2. Return value of `getI()`:

(B) (2 points) Suppose we get rid of register `x` and modify the rule `doComputeStep` and method `getX` as follows.

```

rule doComputeStep if (a > 0 && validx == 0);

```

```

    let b = computeB(a);
    a <= a - b;
    x <= a;
    validx <= 1;
    i <= i + 1;
endrule

method ActionValue#(Bit#(32)) getX() if (validx == 1);
    validx <= 0;
    return x;
    return a;
endmethod

```

Does this change the output sequence of `getX()` of the module?

(circle one) Yes ... No ... Can't tell


(C) (2 points) Ignoring the changes in (C), suppose we modify the guard of `start` in the original code to `(a==0 && validx == 0)`. Does this change the output sequence of `getX()`?

(circle one) Yes ... No ... Can't tell

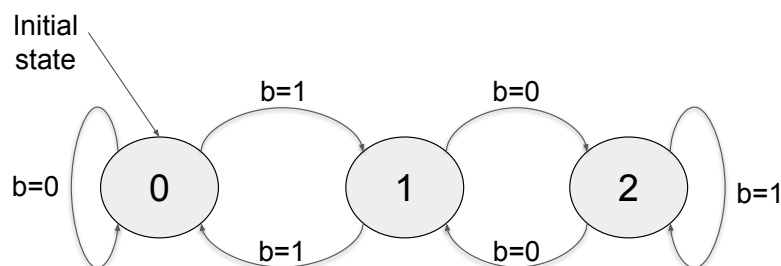Problem 3

Consider a "divisible-by-3" FSM that accepts a binary number entered one bit at a time, most significant bit first. The FSM has a one-bit output that indicates if the number entered so far is divisible by 3.

If the value of the number entered so far is N , then after the digit b is entered, the value of the new number N' is $2N + b$. This leads to the following transition diagram where the states are labeled with the value of $N \bmod 3$.



(A) Construct a truth table for the FSM logic. Inputs include the state bits and the next bit of the number; outputs include the next state bits and the output.

(B) Based on the truth table, implement the FSM using D flip-flops.

Problem 4.

In this problem, we construct a sequential circuit to compute the N^{th} Fibonacci number denoted by F_N . The following recurrence relation defines the Fibonacci sequence.

$$F_0 = 0, F_1 = 1, F_N = F_{N-1} + F_{N-2} \quad \forall \quad N \geq 2$$

The circuit is similar to the GCD circuit discussed in the lecture.

There are two registers **x** and **y** that store the Fibonacci values for two consecutive integers. In addition, a counter register **i** is initialized to $N-1$ and decremented each cycle. The computation stops when register **i** goes down to 0 and the result (F_N) is available in register **x**.

- (A) What are the initial values for registers **x** and **y**?

- (B) Derive the next state computation equations for the three registers.

- (C) Derive the logic for the enable signal that determines when the registers are updated using the next state logic. Note that all three registers are controlled by a single enable signal.

- (D) Implement the sequential circuit using the next state and enable logic derived above.