

Sequential Circuits in Minispec




Lecture Goals

- Learn how to implement sequential circuits in Minispec
 - Design each sequential circuit as a module
 - Modules are similar to FSMs, but are easy to compose
- Explore the advantages of sequential logic over combinational logic
 - Sequential circuits can perform computation over multiple cycles → handle variable amounts of input and/or output and computations that take a variable number of steps

Reminder: Sequential Circuits

State Elements

  
 
- D Flip-Flop (DFF): State element that samples its data (D) input at the rising edge of the clock
- Common DFF enhancements:
 - Reset circuit to set initial value
 - Write-enable circuit to optionally retain current value
- Register: Group of DFFs
 - Stores multi-bit values



Reminder: Sequential Circuits

Finite State Machines

 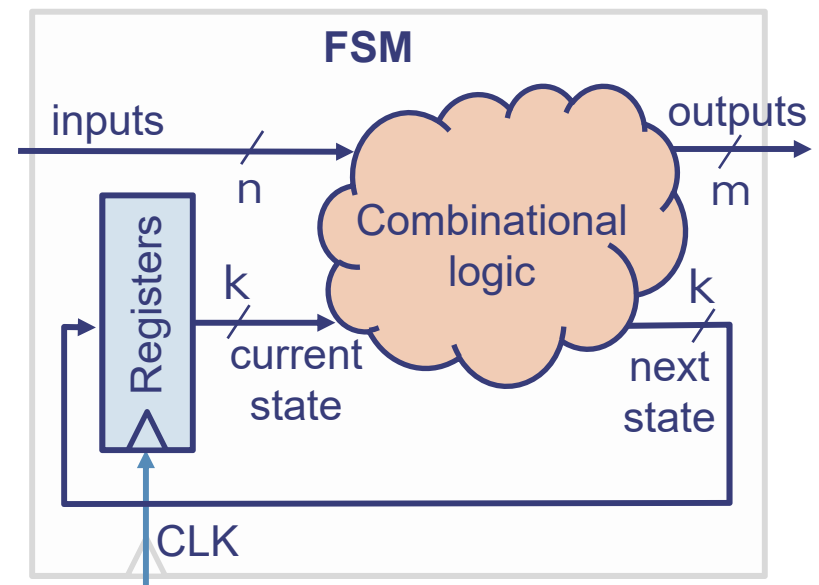- Synchronous sequential circuits: All state kept in registers driven by the same clock
- This allows discretizing time into cycles and abstracting sequential circuits as **finite state machines (FSMs)**
- FSMs can be described with **state-transition diagrams** or truth tables




Problem: FSMs Don't Compose

- Key strategy: Build large circuits from smaller ones
- Problem: Wiring up FSMs can introduce combinational cycles

```
fsm Inner;  
  Reg r;  
  out = in ^ r.q;  
  ...
```

 
```
fsm Outer;  
  Inner s;  
  s.in = !s.out;  
  ...
```



- Most hardware description languages work this way
 - Just wire up FSMs however you want!
 - Got a cycle? `~_(\ツ)_/~`
 - If curious, read [“Verilog is weird”](#), Dan Luu, 2013

Modules



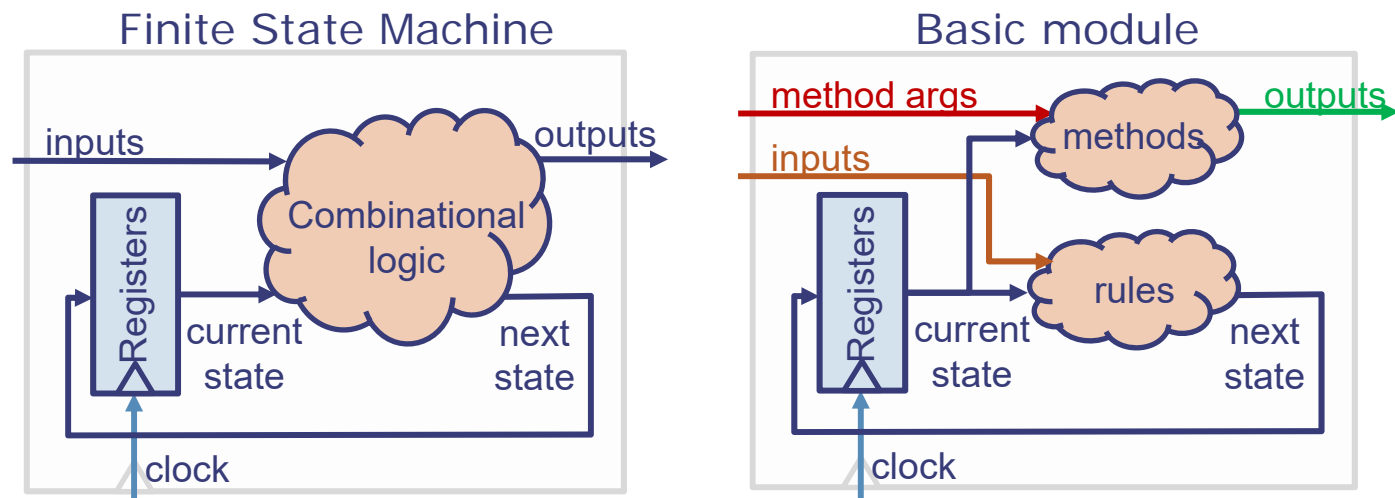
- Minispec modules add some structure to FSMs to make them composable



- Modules separate the combinational logic to compute the outputs and the next state
 - Methods** compute outputs
 - Rules** compute next state
 - Methods and rules use separate inputs

Reminder: Two-Bit Counter

Prev State	NextState	
q1q0	inc = 0	inc = 1
00	00	01
01	01	10
10	10	11
11	11	00

   

Two-Bit Counter in Minispec

```
module TwoBitCounter;  
  Reg#(Bit#(2)) count(0);
```

Instantiates a 2-bit register named count with initial value 0

```
  method Bit#(2) getCount  
    = count;
```

getCount method produces the output

```
  input Bool inc;
```

```
  rule increment;  
    if (inc)  
      count <= count + 1;
```

increment rule computes the next state: if inc input is True, updates count to count + 1

```
  endrule  
endmodule
```

Rules execute automatically every cycle

The Reg#(T) Module

- Reg#(T) is a register of values of type T
 - e.g., Reg#(Bool) or Reg#(Bit#(16)), not Reg#(16)
- Register writes use a special register assignment operator: \leq
 - e.g., `count \leq count + 1`, not `count = count + 1`
- \leq has two key differences with $=$
 1. $=$ assigns to variable immediately, but \leq updates register at the end of the cycle
 2. Registers can be written at most once per cycle

Composing Modules

```
module FourBitCounter;  
  TwoBitCounter lower;  
  TwoBitCounter upper;
```

Instantiates a TwoBitCounter
submodule named lower
(stores lower 2 bits of our count)

```
  method Bit#(4) getCount =  
    {upper.getCount, lower.getCount};
```

```
input Bool inc;
```

```
rule increment;
```

increment rule sets the inputs
of lower and upper submodules

```
  lower.inc = inc;
```

```
  upper.inc = inc && (lower.getCount == 3);
```


```
endrule
```

```
endmodule
```


Increment upper counter when lower
counter rolls over from 3 to 0

Module Components

Basic module (with registers only)

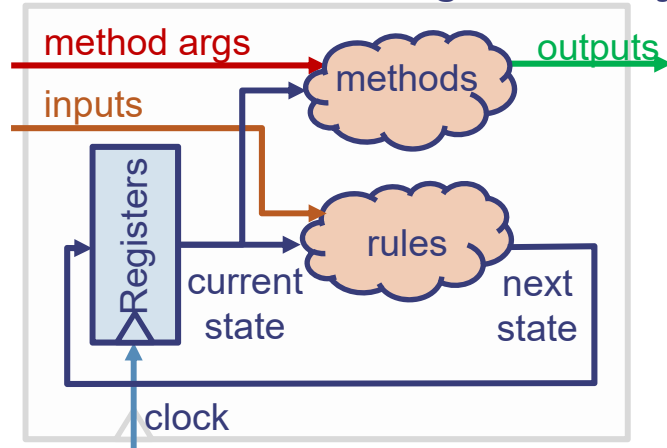

General module (with other submodules)

 

1. **Submodules**, which can be registers or other user-defined modules to allow composition of modules
2. **Methods** produce outputs given some input arguments and the current state
3. **Rules** produce the next state and submodule inputs given some external inputs and the current state
4. **Inputs** represent external inputs controlled by the enclosing module

Modules Compose Cleanly

- In 6.004 we will only use **strict hierarchical composition**, which obeys two restrictions:
 1. Each module interacts only with its own submodules
 2. Methods do not read inputs (only their own arguments)
- These conditions guarantee two nice properties:
 1. It is impossible to get combinational cycles
 2. Very simple semantics: System behaves as if rules fire sequentially, outside-in (i.e., first the outermost module, then its submodules, and so on)
- Minispec supports non-hierarchical composition (with similar guarantees), but we will not use it

Simulating and Testing Modules

- Modules can be simulated/tested with **testbenches**
 - Another module that uses tested module as a submodule
 - Drives its inputs through a sequence of test cases
 - Checks that outputs are as expected
 - **System functions** let testbench modules output results and control simulation
 - `$display` to print output
 - `$finish` to terminate simulation
 - System functions have no hardware meaning, are ignored when synthesized
- ```
module FourBitCounterTest;
 FourBitCounter counter;
 Reg#(Bit#(6)) cycle(0);

 rule test;
 // Increment only on odd cycles
 counter.inc = (cycle[0] == 1);



 // Print the current count
 $display("[cycle %d] getCount = %d",
 cycle, counter.getCount);

 // Terminate after 32 cycles
 cycle <= cycle + 1;
 if (cycle >= 32) $finish;
 endrule
endmodule
```

# Multi-Cycle Computations
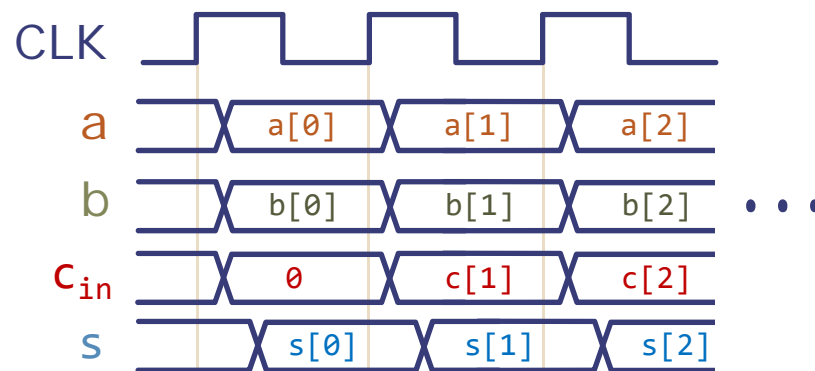 
# Time is More Flexible Than Space

- Sequential circuits can implement more computations than combinational circuits
  - Variable amount of input and/or output
  - Variable number of steps
- Example: Build a circuit that adds two numbers of arbitrary length
  - Combinational: Can't, inputs/outputs must have fixed width
  - Sequential: Trivial, add one digit per cycle:



# Example: GCD

---

- Euclid's algorithm efficiently computes the greatest common divisor (GCD) of two numbers:

```
def gcd(a, b):
```

```
 x = a
```

```
 y = b
```

```
 while x != 0:
```

```
 if x >= y: # subtract
```

```
 x = x - y
```

```
 else: # swap
```

```
 (x, y) = (y, x)
```

```
 return y
```

Example: gcd(15, 6)

x: 15

y: 6

9

6

*subtract*

3

6

*subtract*

6

3

*swap*

3

3

*subtract*

0

3


*subtract*

*result*

- Takes a variable number of steps
- Approach: Build a sequential circuit that performs one iteration of the while loop per cycle



# GCD Circuit

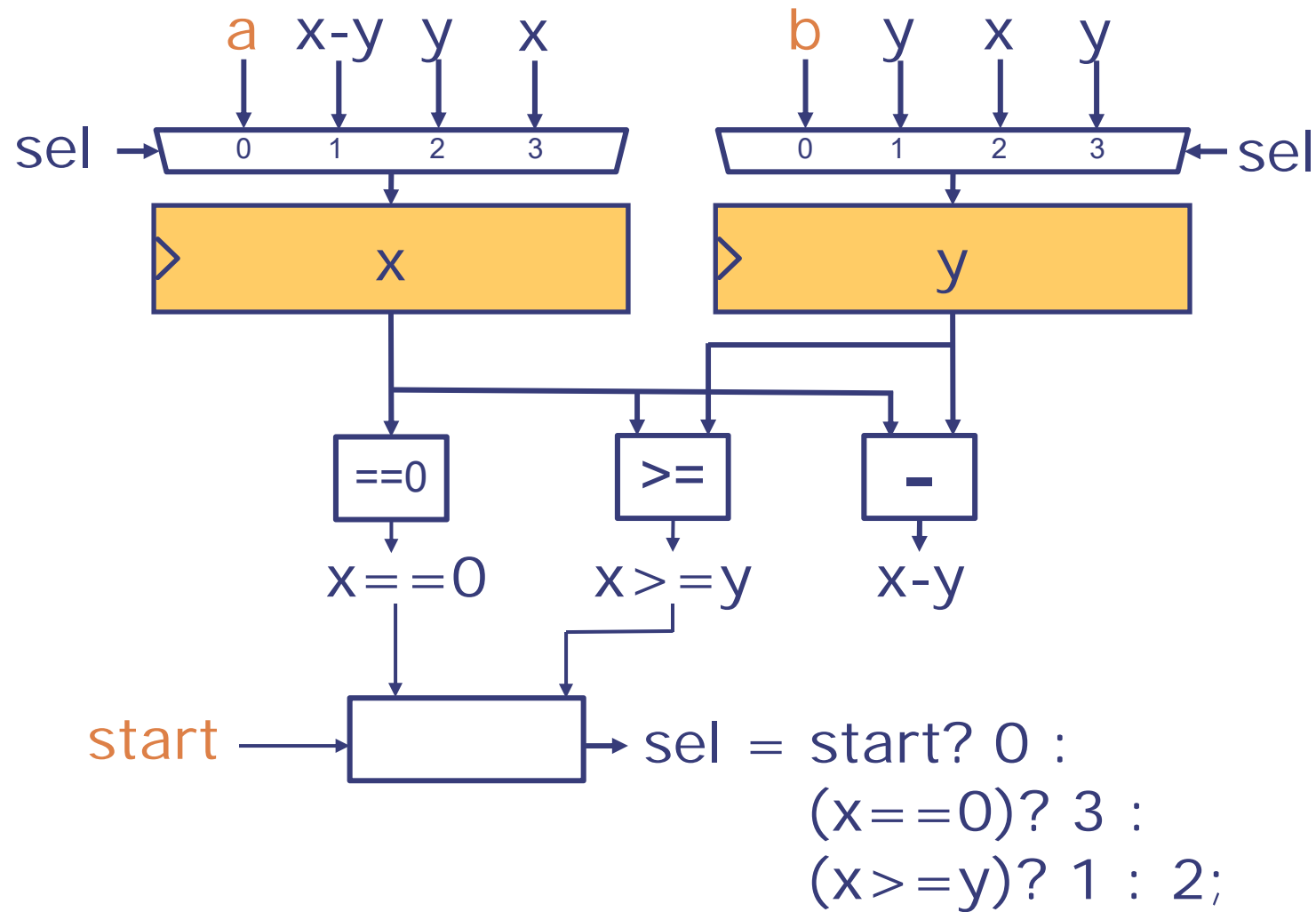

# GCD in Minispec

## First version

---

```
typedef Bit#(32) Word;
module GCD;
 Reg#(Word) x(1);
 Reg#(Word) y(0);
 input Bool start;
 input Word a;
 input Word b;
 rule gcd;
 if (start) begin
 x <= a; y <= b;
 end else if (x != 0) begin
 if (x >= y) begin // subtract
 x <= x - y;
 end else begin // swap
 x <= y; y <= x;
 end
 end
 endrule
 method Word result = y;
 method Bool isDone = (x == 0);
endmodule
```

New GCD computation is started by setting start input to True and passing arguments through inputs a and b

Several cycles later, the module will signal it has finished through isDone. Then, the result gcd(a,b) will be available through the result method.

# Designing Good Module Interfaces

---

- The previous GCD module has a poor interface
  - Easy to misuse. *Why?*
    - *e.g., may forget to check isValid and read wrong result!*
  - Tedious to use. *Why?*
    - *e.g., if start is False, we still have to set the a and b inputs, even though they are not used!*
- To design good interfaces,  
    **group related inputs and outputs**
  - In our case, GCD should have:
    - A single output that is either invalid or a valid result
    - A single input that is either no arguments or arguments
  - This requires we learn about one last type...

# The Maybe Type

---

- `Maybe#(T)` represents an **optional** value of type `T`
    - Either `Invalid` and no value, or `Valid` and a value
  - Possible implementation: A value + a valid bit
- ```
typedef struct { Bool valid; T value; } Maybe#(type T);
```
 - Although we could implement our own, optional values are so common that `Maybe#(T)` has a few built-in operations

```
Maybe#(Word) x = Invalid;    // no need to give value!  
Maybe#(Word) y = Valid(42);  // must specify a value
```

```
if (isValid(y))                // check validity  
    Word z = fromMaybe(?, y);  // extract valid value
```

Improved GCD Module

Using Maybe Types

```
typedef struct {Word a; Word b;} GCDArgs;
module GCD;
  Reg#(Word) x(1);
  Reg#(Word) y(0);
  input Maybe#(GCDArgs) in;
  rule gcd;
    if (isValid(in)) begin
      let args = fromMaybe(?, in);
      x <= args.a; y <= args.b;
    end else if (x != 0) begin
      if (x >= y) begin // subtract
        x <= x - y;
      end else begin // swap
        x <= y; y <= x;
      end
    end
  endrule
  method Maybe#(Word) result =
    (x == 0)? Valid(y) : Invalid;
endmodule
```

New GCD computation is started by setting a Valid input in (which always includes a and b)

When GCD computation finishes, result becomes a Valid output

Summary

- Modules implement FSMs in a composable way
 - Extra structure to FSMs: Combinational logic split into rules (produce next state) and methods (produce outputs)
 - Clean hierarchical composition: No combinational cycles, system behaves as if rules execute outside-in
- Sequential circuits can implement more computations than combinational circuits
 - Variable amount of input and/or output
 - Variable number of steps
- To build simple, easy-to-use module interfaces, group related inputs and outputs

Thank you!

Next lecture:
Arithmetic Pipelines