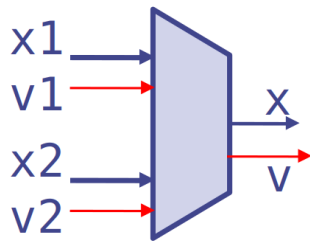


## 6.004 Recitation 11

### L11 – Hardware Synthesis From Bluespec

#### Handling multiple input sources

There are many situations where we would like a module in our circuit to be able to receive its input from multiple different data sources. In these situations, we use the following **mux-like structure** to parse the input sources into a single output.



$$x = (v1 \ \& \ x1) \mid (v2 \ \& \ x2)$$
$$v = v1 \mid v2$$

As long as the Bluespec compiler ensures that only 1  $v_i$  value is true at any time, then this module produces the corresponding  $x_i$  value. We can then use the output of  $v$  to detect that output  $x$  is valid.

#### Registers: primitive state modules

Registers are an essential module used to store state across clock cycles. They adhere to the following interface:

```
interface Reg#(type t);  
  method Action _write(t x);  
  method t _read;  
endinterface
```

Registers also include some special syntax in Bluespec, namely

- $x \leq v$       With Register  $x$  is equivalent to  $x.write(v)$
- $x$             With Register  $x$  is equivalent to  $x.read$

## Method Interfaces

Every method compiled by Bluespec has can have 3 key interfaces:

- **Enable** is an input that when set to true activates the module
- **Ready** is an output that states whether the module can be activated
- **Data** can be either input or output data interfaces

Not every method has to have all of them, but they dictate when and how a method will interact externally. In Bluespec, the following statements are true in general


- Each *method* has an output **ready** wire
- Each *method* may have 0 or more input data wires
- Each *Action method* and *ActionValue method* has an input **enable** wire
- Each *value method* and *ActionValue method* has an output data wire
- An *Action method* has no output data wire

*Note:* For Registers in particular, the **ready** wires for both `_write` and `_read` are always true!
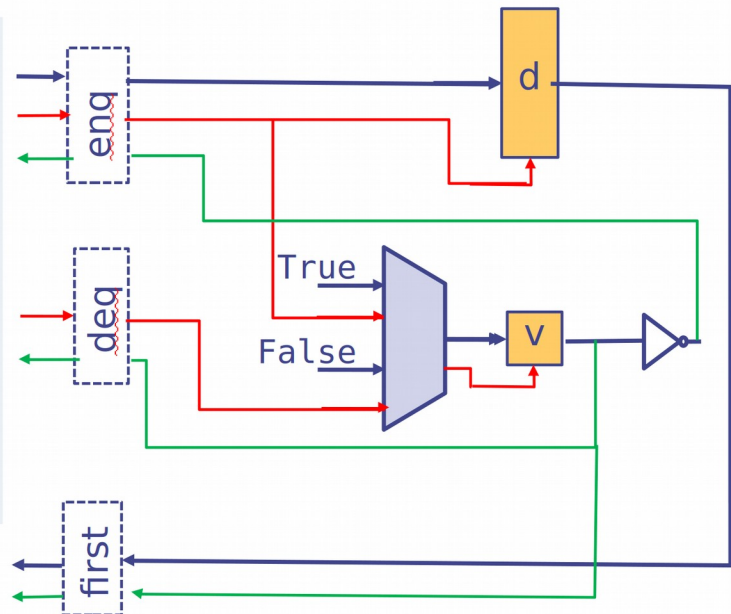
## Guards and Ready signals

In Bluespec, the **ready** signal for a method is constructed from all explicit and implicit (inherited from other methods called within the method) guards of that method. Consider the following interface and circuit from lecture:

```
module mkFifo (Fifo#(1, t));  
  Reg#(t)    d <- mkRegU;  
  Reg#(Bool) v <-  
    mkReg(False);  
  method Action enq(t x) if (!  
    v);  
    v <= True; d <= x;  
  endmethod  
  method Action deq if (v);  
    v <= False;  
  endmethod  
  method t first if (v);  
    return d;  
  endmethod  
endmodule
```




It is apparent from the green **ready** wires that the ready signals for `enq`, `deq`, and `first` correspond directly with the guards, with them being `!v`, `v`, and `v`, respectively.

## Practice Synthesis

Given the following interfaces for a function streaming module, implement the rules `invokeFunction`, which takes an element from `inQ` and passes it to module `f`'s `begin` method, and `getResult`, which gets a value from `f`'s `result` method and enqueues it into `outQ`. Then on the next page, draw a synthesized circuit for the streaming module

```
interface f#(type t);  
  method Action begin(t x);  
  method ActionValue#(t) result;  
endinterface
```
 
```
interface Fifo#(type t);  
  method Action enq(t x);  
  method ActionValue#(t) pop;  
endinterface
```



```
rule invokeFunction;  
  let x = inQ.pop;  
  f.begin(x);  
endrule
```

```
rule getResult;  
  let x <- f.result;  
  outQ.enq(x);  
endrule
```

## Synthesized Circuit:

