

Complex Combinational circuits in Bluespec

Arvind

Computer Science & Artificial Intelligence Lab
M.I.T.

Reminders:

Lab 3 due today

Quiz 1 Review: Tuesday March 5, 7:30-9PM 6-120

Quiz 1: March 7th 7:30-9:30PM

Bluespec is for describing circuits


- Bluespec is like a language for drawing pictures of interconnected boxes
- Boxes happen to be Boolean gates with inputs and outputs
- However, unlike ordinary pictures, our boxes, i.e., gates, have computational meaning, and therefore, we can ask what values a circuit would produce on its output lines, given a specific set of values on its input lines
- Even though the primary purpose of the Bluespec compiler is to synthesize a network of gates, the ability to simulate the functionality of the resulting circuit is extremely important

Bluespec: Gate synthesis versus simulation 2-bit adder

```
function Bit#(3) add2(Bit#(2) x, Bit#(2) y);  
  Bit#(2) s = 0;      Bit#(3) c = 0;  
  c[0] = 0;  
  Bit#(2) cs0 = fa(x[0], y[0], c[0]);  
  s[0] = cs0[0];      c[1] = cs0[1];  
  Bit#(2) cs1 = fa(x[1], y[1], c[1]);  
  s[1] = cs1[0];      c[2] = cs1[1];  
  return {c[2],s};  
endfunction
```


simulate

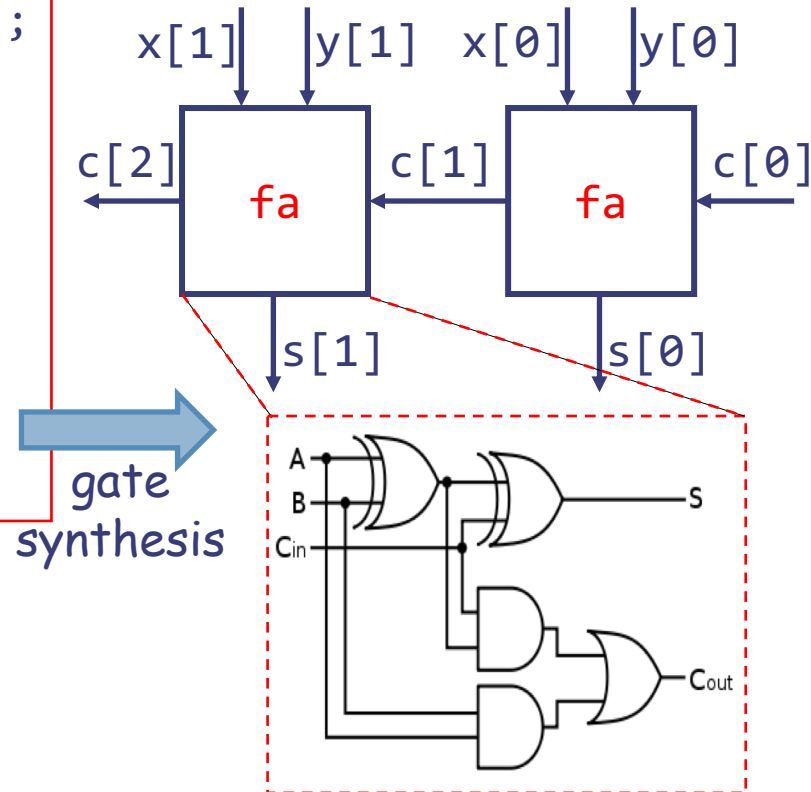- $\text{add2}(2'b11, 2'b01) \Rightarrow 3'b100$
- $\text{add2}(2'b01, 2'b01) \Rightarrow 3'b010$



Caution: In spite of the fact that Bluespec programs, like programs in other software languages, produce outputs given inputs, the purpose of Bluespec programs is to describe circuits

Compiling Bluespec into circuits

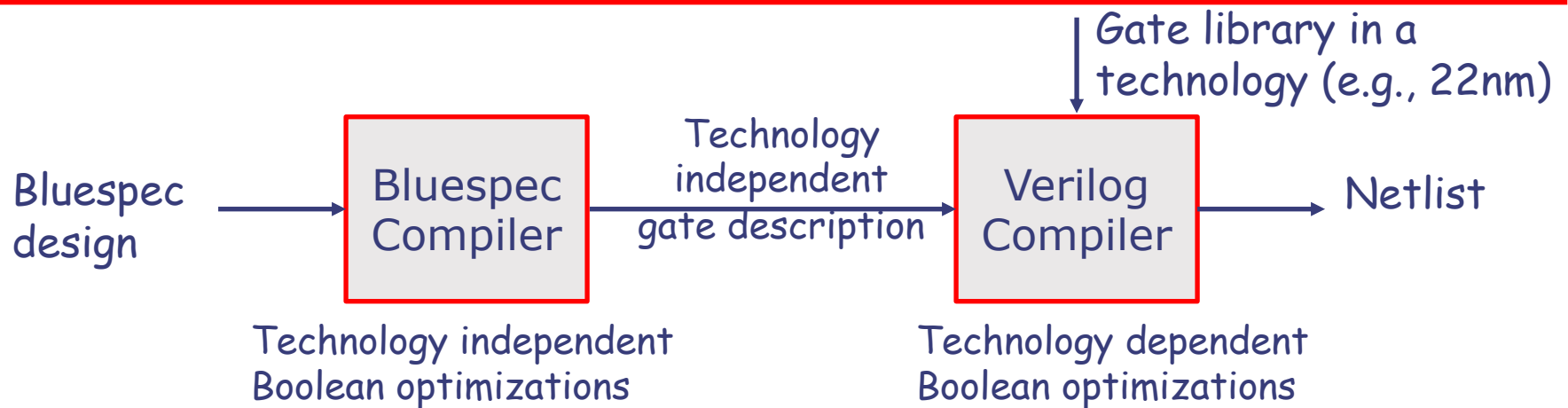

- *Static elaboration:* Bluespec compiler eliminates all constructs which have no direct hardware meaning
 - All data structures are converted into bit vectors
 - Loops are unfolded
 - Functions are in-lined
 - What remains is an acyclic graph of Boolean gates
 - The compiler complains if it detects a cycle in your circuit

32-bit Ripple-Carry Adder (RCA)

- We could have written the chain of RCA explicitly, but we can also use loops!

```
function Bit#(33) add32(Bit#(32) x, Bit#(32) y, Bit#(1) c0);  
    Bit#(32) s = 0;  
    Bit#(33) c = 0;  
    c[0] = c0;  
    for (Integer i=0; i<32; i=i+1) begin  
        Bit#(2) cs = fa(x[i],y[i],c[i]);  
        c[i+1] = cs[1];  
        s[i] = cs[0];  
    end  
    return {c[32],s};  
endfunction
```

Now we discuss how the gates are generated (synthesized) from a loop

Back to our 32-bit ripple carry adder

```
for(Integer i=0; i<32; i=i+1) begin
    Bit#(2) cs = fa(x[i], y[i], c[i]);
    c[i+1] = cs[1];
    s[i] = cs[0];
end
```

Unfold the loop


```
cs = fa(x[0], y[0], c[0]);
c[1] = cs[1];
s[0] = cs[0];
cs = fa(x[1], y[1], c[1]);
c[2] = cs[1];
s[1] = cs[0];
...
cs = fa(x[31], y[31], c[31]);
c[32] = cs[1];
s[31] = cs[0];
```

cs in the loop body is a local variable. Hence each of these cs refers to a different value. We could have named them cs0, ... cs31.

Loops to gates

```
cs0 = fa(x[0], y[0], c[0]); c[1]=cs0[1]; s[0]=cs0[0];  
cs1 = fa(x[1], y[1], c[1]); c[2]=cs1[1]; s[1]=cs1[0];  
...  
cs31 = fa(x[31], y[31], c[31]);  
c[32] = cs31[1]; s[31] = cs31[0];
```

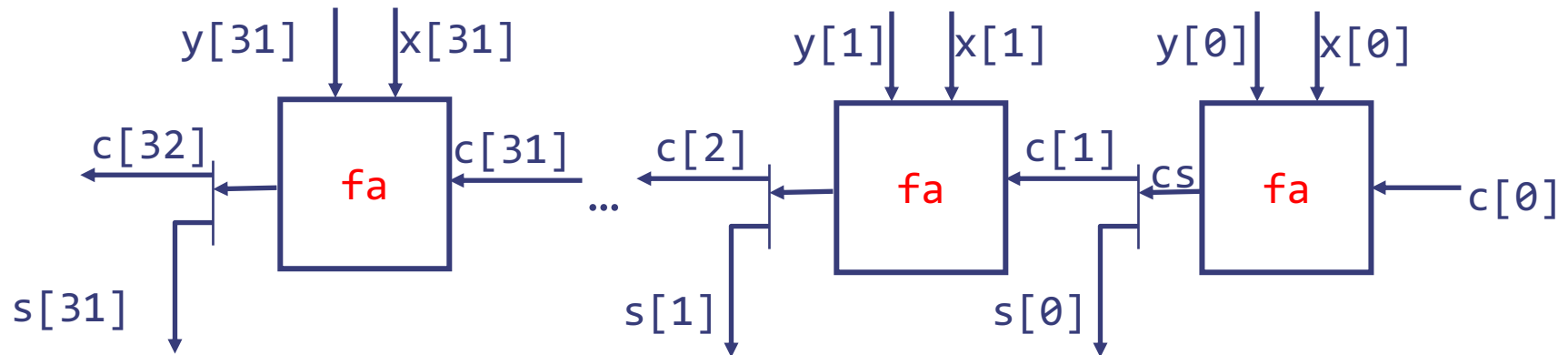Unfolded loop defines an acyclic wiring diagram



Each instance of function **fa** is replaced by its body

Multiplication by repeated addition

b Multiplicand 1101 (13)
a Multiplier * 1011 (11)

tp
m0 + 0000
+ 1101
tp
m1 + 01101
+ 1101
tp
m2 + 100111
+ 0000
tp
m3 + 0100111
+ 1101
tp
10001111 (143)

The diagram illustrates the process of multiplying 1101 (13) by 1011 (11) using repeated addition. The multiplier bits are 1, 0, 1, 1 from left to right. For each bit, the multiplicand (1101) is added to the running total (tp) if the bit is 1, or 0 is added if the bit is 0. The running total is shifted one position to the left for each step. The final result is 10001111 (143).

At each step we add either 1101 or 0 to the result depending upon a bit in the multiplier

$$m_i = (a[i] == 0) ? 0 : b;$$

We also shift the result by one position at every step


Notice, the first addition is unnecessary because it simply yields m0

Multiplication by repeated addition circuit

b Multiplicand 1101 (13)
a Multiplier * 1011 (11)

tp		0000	
m0	+	1101	
tp		01101	
m1	+	1101	
tp		100111	
m2	+	0000	
tp		0100111	
m3	+	1101	
tp		10001111	(143)

$m_i = (a[i] == 0) ? 0 : b;$

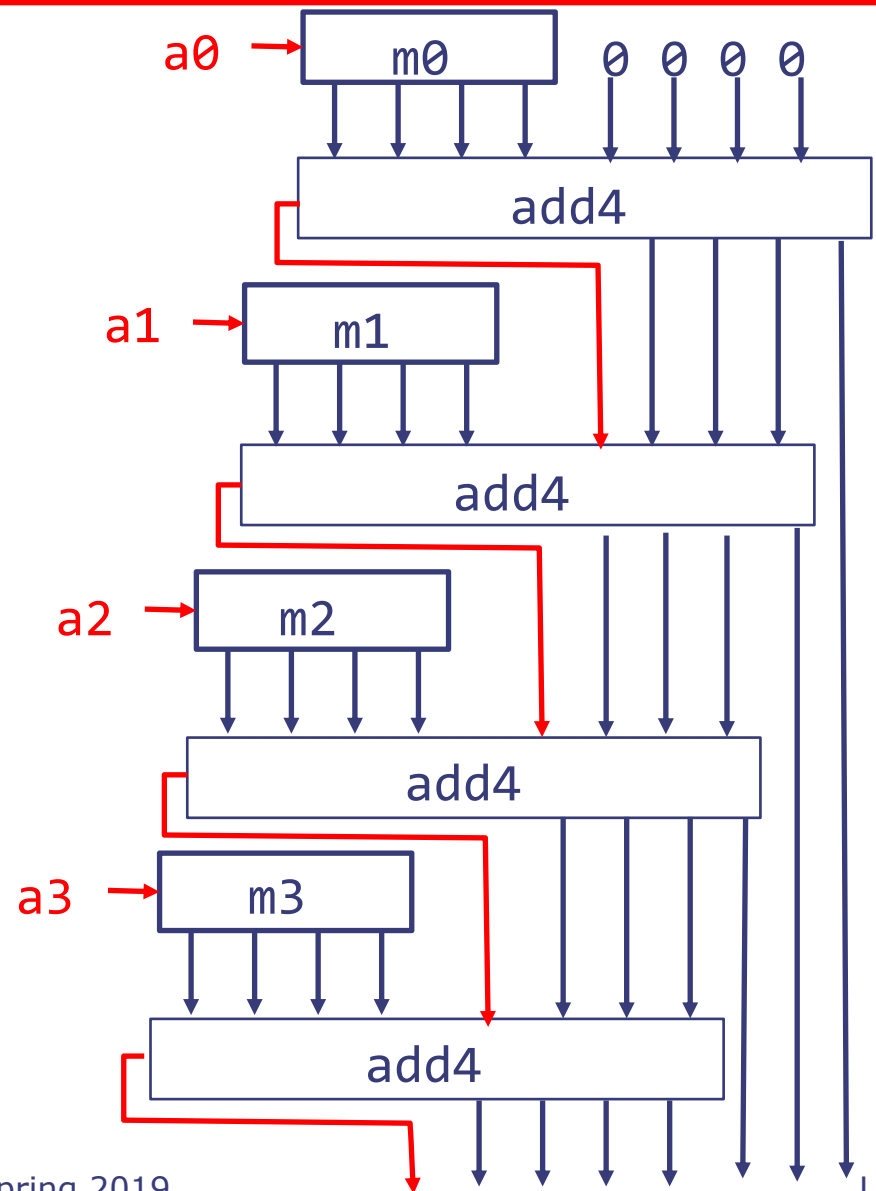

Combinational 32-bit multiply

```
function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
  Bit#(32) tp = 0;
  Bit#(32) prod = 0;
  for(Integer i = 0; i < 32; i = i+1)
  begin
    Bit#(32) m    = (a[i]==0)? 0 : b;
    Bit#(33) sum  = add32(m,tp,0);
    prod[i]      = sum[0];
    tp           = sum[32:1];
  end
  return {tp,prod};
endfunction
```

This circuit uses
32 add32 circuits



Lot of gates!

Analysis of 32-bit multiply

```
function Bit#(64) mul32(Bit#(32) a, Bit#(32) b);
  Bit#(32) tp = 0;
  Bit#(32) prod = 0;
  for(Integer i = 0; i < 32; i = i+1)
  begin
    Bit#(32) m    = (a[i]==0)? 0 : b;
    Bit#(33) sum  = add32(m,tp,0);
    prod[i]      = sum[0];
    tp           = sum[32:1];
  end
  return {tp,prod};
endfunction
```

- ◆ Can we design a faster adder?
 - yes!
- ◆ Can we reuse the adder circuit and reduce the size of the multiplier
 - *stay tuned ...*

◆ Long chains of gates

- 32-bit multiply has 32 ripple carry adders in sequence!
- 32-bit ripple carry adder has a 32-long chain of gates

Take home problem: What is the propagation delay of mul32 in terms of FA delays?

n-bit Ripple-Carry Adder

```
function Bit#(n+1) addN(Bit#(n) x, Bit#(n) y, Bit#(1) c0);  
    Bit#(n) s = 0;  
    Bit#(n+1) c = 0;  
    c[0] = c0;  
    for (Integer i=0; i<n; i=i+1) begin  
        let cs = fa(x[i],y[i],c[i]);  
        c[i+1] = cs[1];  
        s[i] = cs[0];  
    end  
    return {c[n],s};  
endfunction
```

Now can instantiate different sized adders by specifying n

Unfortunately, there are several subtle type errors in this program - we will fix them one by one

Introduction to Types in Bluespec

Types

- Every expression in a Bluespec program has a type
- A type is a *grouping* of values, examples
 - `Bit#(16)` // 16-bit wide bit-vector (16 is a numeric type)
 - `Bool` // 1-bit value representing True or False
 - `Vector#(16, Bit#(8))` // Vector of size 16 containing `Bit#(8)`'s
- A type declaration can be parameterized by other types using the syntax ``#'`, for example
 - `Bit#(n)` represents *n* bits, e.g., `Bit#(8)`, `Bit#(32)`, ...
 - `Tuple2#(Bit#(8), Integer)` represents a pair of 8-bitvector and an integer.
 - `function Bit#(8) fname (Bit#(8) arg)` represents a function from `Bit#(8)` to `Bit#(8)` values
- A *type name* always begins with a capital letter, while a *variable identifier* begins with a small letter

Type synonyms

```
typedef Bit#(8) Byte;
```

```
typedef Bit#(32) Word;
```

```
typedef Tuple2#(a,a) Pair#(type a);
```

type variable

```
typedef 32 DataSize;
```

numeric type

```
typedef Bit#(DataSize) Data;
```

Enumerated types

A very useful typing concept

- Suppose we have a variable `c` whose values can represent three different colors
 - Declare the type of `c` to be `Bit#(2)` and adopt the convention that 00 represents Red, 01 Blue and 10 Green
- A better way is to create a new type called `Color`:
`typedef enum {Red, Blue, Green}` *Why is this way better?*
`Color deriving(Bits, Eq);`
- Bluespec compiler automatically assigns a bit representation to the three colors and provides a function to test whether two colors are equal
- If you do not use “deriving” then you will have to specify your own encoding and equality function

*Types prevent us from
mixing colors with raw bits*

Type checking

- The Bluespec compiler checks if all the declared types are used consistently

```
function Bit#(23) fa(Bit#(1) a, Bit#(1) b, Bit#(1) c_in);  
    Bit#(2) ab = ha(a, b);  
    Bit#(2) abc = ha(ab[0], c_in);  
    Bit#(1) c_out = ab[1] | abc[1];  
    return {c_out, abc[0]};  
endfunction
```

The compiler will flag this as an error because {c_out, abc[0]} is Bit#(2)

- In fact, the compiler can reduce the programmer's burden by deducing some types and not asking for explicit type declarations

⇒ The "let" syntax

“let” syntax

```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b, Bit#(1) c_in);  
    Bit#(2) ab  = ha(a, b);  
    Bit#(2) abc = ha(ab[0], c_in);  
    Bit#(1) c_out = ab[1] | abc[1];  
    return {c_out, abc[0]};  
endfunction
```

```
function Bit#(2) fa(Bit#(1) a, Bit#(1) b, Bit#(1) c_in);  
    let ab  = ha(a, b);  
    let abc = ha(ab[0], c_in);  
    let c_out = ab[1] | abc[1];  
    return {c_out, abc[0]};  
endfunction
```

Type of ab and abc can be deduced from the type of ha

“let” syntax is very convenient, we will use it extensively in the slides.

Fixing the type errors

Parameterized Ripple-Carry Adder

```
function Bit#(n+1) addN(Bit#(n) x, Bit#(n) y, Bit#(1) c0);  
  Bit#(n) s = 0;  
  Bit#(n+1) c = 0;  
  c[0] = c0;  
  for (Integer i=0; i<n; i=i+1) begin  
    let cs = fa(x[i],y[i],c[i]);  
    c[i+1] = cs[1];  
    s[i] = cs[0];  
  end  
  return {c[n],s};  
endfunction
```

- n is numeric type and Bluespec does not allow arithmetic on types, e.g., $n+1$, $i < n$, $c[n]$ are illegal!

Fixing the type errors

valueOf(n) versus n

- Each expression has a *type* and a *value*, and these two come from entirely disjoint worlds
- n in $\text{Bit\#}(n)$ is a *numeric type* variable and resides in the types world
- Sometimes we need to use values from the types world in actual computation. The function `valueOf` extracts the integer from a numeric type
 - Thus,
 - $i < n$ is not type correct
 - $i < \text{valueOf}(n)$ is type correct

Fixing the type errors

TAdd#(n,1) versus n+1

- Sometimes we need to perform operations in the types world that are very similar to the operations in the value world
 - Examples: Addition, Multiplication, Logarithm base 2, ...
- Bluespec defines a few special operators in the types world for such operations
 - `TAdd#(m,n)`, `TSub#(m,n)`, `TMul#(m,n)`, `TDiv#(m,n)`, `TLog#(n)`, `TExp#(n)`, `TMax#(m,n)`, `Tmin#(m,n)`
 - Thus,
 - `Bit#(n+1)` is not type correct
 - `Bit#(TAdd#(n,1))` is type correct

Parameterized Ripple-Carry Adder

corrected

```
function Bit#(TAdd#(n,1)) addN(Bit#(n) x, Bit#(n) y,  
                                Bit#(1) c0);
```

```
    Bit#(n) s = 0;
```

```
    Bit#(TAdd#(n,1)) c;
```

```
    c[0] = c0;
```

```
    let valn = valueOf(n);
```

```
    for (Integer i=0; i<valn; i=i+1) begin
```

```
        let cs = fa(x[i], y[i], c[i]);
```

```
        c[i+1] = cs[1];
```

```
        s[i] = cs[0];
```

```
    end
```

```
    return {c[valn],s};
```

```
endfunction
```

types world
equivalent of n+1

Lifting a type into
the value world

Takeaway

- Once we define a combinational circuit, we can use it repeatedly to build larger circuits
- Bluespec compiler, because of the type signatures of functions, prevents us from connecting functions and gates in obviously illegal ways
- We can use loop constructs and functions to express combinational circuits, but all loops are unfolded and functions are in-lined during the compilation phase
- *Advanced concept:* We can also write parameterized circuits in Bluespec, for example an n-bit adder. Once n is specified, the correct circuit is automatically generated

The best way to learn about types is to try writing a few expressions and feeding them to the compiler